
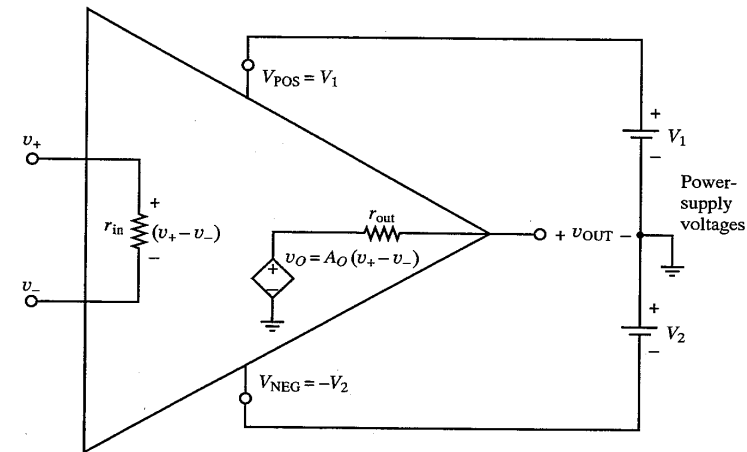


Operational Amplifiers


- An operational amplifier (called op-amp) is a specially-designed amplifier in bipolar or CMOS (or BiCMOS) with the following typical characteristics:
 - Very high gain (10,000 to 1,000,000)
 - Differential input
 - Very high (assumed infinite) input impedance
 - Single ended output
 - Very low output impedance
 - Linear behavior (within the range of $V_{\text{NEG}} < v_{\text{out}} < V_{\text{POS}}$)
- Op-amps are used as generic “black box” building blocks in much analog electronic design
 - Amplification
 - Analog filtering
 - Buffering
 - Threshold detection
- Chapter 2 treats the op-amp as a black box; Chapters 8-12 cover details of op-amp design
 - Do not really need to know all the details of the op-amp circuitry in order to use it

Generic View of Op-amp Internal Structure


- An op-amp is usually comprised of at least three different amplifier stages (see figure)
 - Differential amplifier input stage with gain $a_1(v_+ - v_-)$ having inverting & non-inverting inputs
 - Stage 2 is a “Gain” stage with gain a_2 and differential or singled ended input and output
 - Output stage is an emitter follower (or source follower) stage with a gain = ~ 1 and single-ended output with a large current driving capability
- Simple Op-Amp Model (lower right figure):
 - Two supplies V_{POS} and V_{NEG} are utilized and always assumed (even if not explicitly shown)
 - An input resistance r_{in} (very high)
 - An output resistance r_{out} (very low) in series with output voltage source v_o
 - Linear Transfer function is $v_o = a_1 a_2 (v_+ - v_-) = A_o (v_+ - v_-)$ where A_o is open-loop gain
 - v_o is clamped at V_{POS} or V_{NEG} if $A_o (v_+ - v_-) > V_{POS}$ or $< V_{NEG}$, respectively

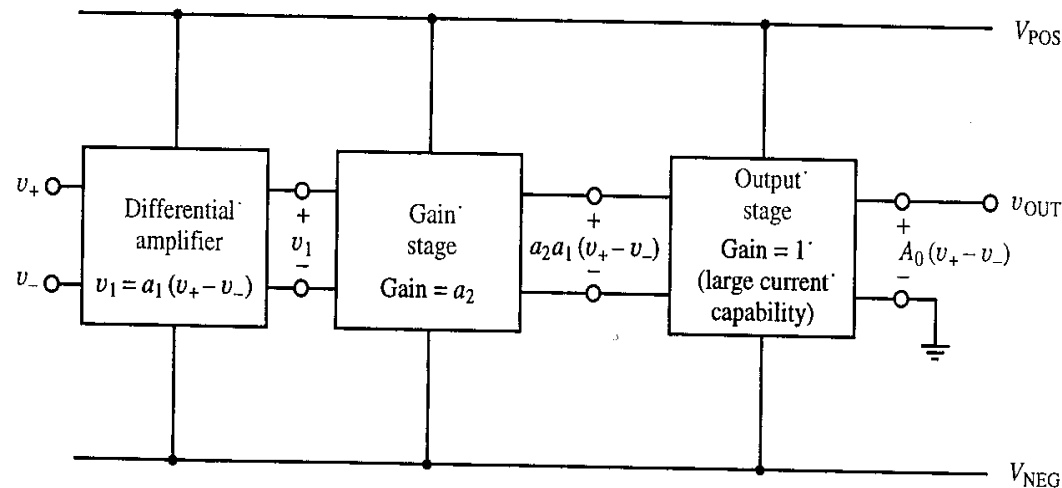

Ideal Op-amp Approximation

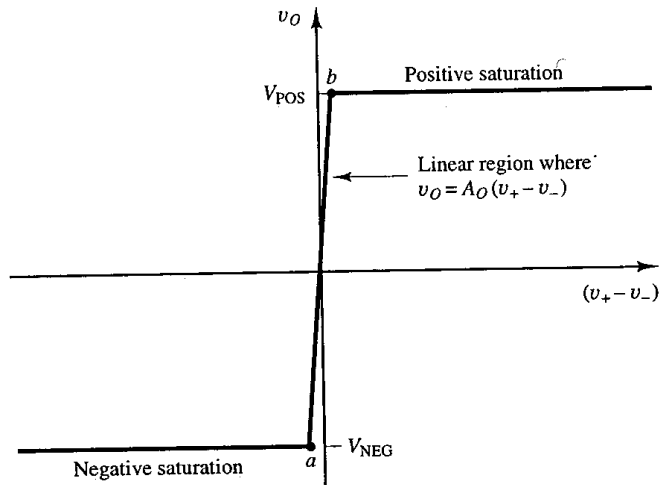


- Because of the extremely high voltage gain, high input resistance, and low output resistance of an op-amp, we use the following ideal assumptions:
 - The saturation limits of v_o are equal V_{POS} & V_{NEG}
 - If $(v_+ - v_-)$ is slightly positive, v_o saturates at V_{POS} ; if $(v_+ - v_-)$ is slightly negative, v_o saturates at V_{NEG}
 - If v_o is not forced into saturation, then $(v_+ - v_-)$ must be very near zero and the op-amp is in its linear region (which is usually the case for negative feedback use)
 - The input resistance can be considered **infinite** allowing the assumption of zero input currents
 - The output resistance can be considered to be **zero**, which allows V_{out} to equal the internal voltage v_o
- The idealized circuit model of an op-amp is shown at the left-bottom figure
- The transfer characteristic is shown at the left-top
- Op-amps are typically used in negative feedback configurations, where some portion of the output is brought back to the negative input v_-

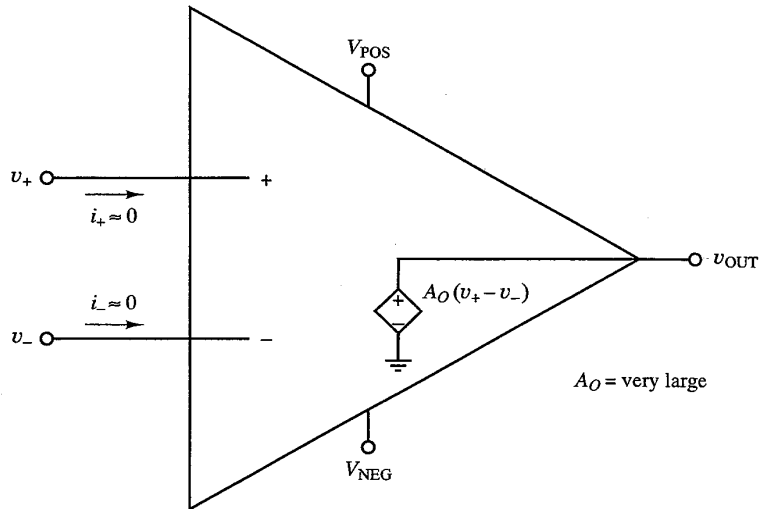


Linear Op-amp Operation: Non-Inverting Use

Fig. 2.5 (a) Noninverting amplifier configuration; (b) block diagram of circuit's operational function.

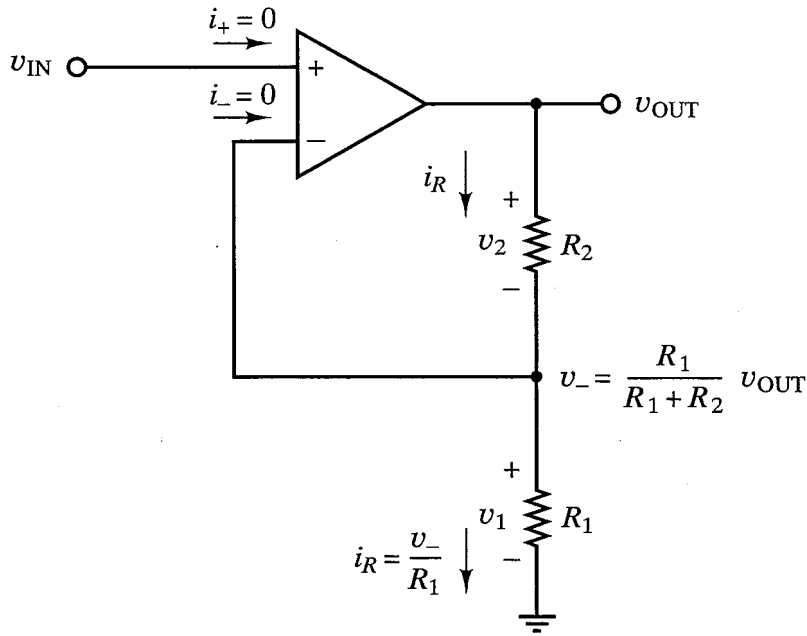

(a)

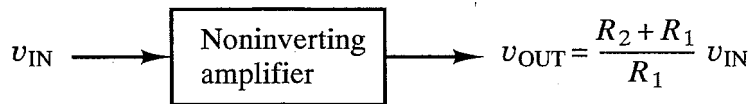

(b)

- An op-amp can use *negative feedback* to set the closed-loop gain as a function of the circuit external elements (resistors), independent of the op-amp gain, as long as the internal op-amp gain is very high
- Shown at left is an ideal op-amp in a non-inverting configuration with negative feedback provided by voltage divider R_1, R_2
- Determination of closed-loop gain:
 - Since the input current is assumed zero, we can write $v_- = \mathbf{R1/(R1 + R2)}v_{OUT}$
 - But, since $v_+ \approx v_-$ for the opamp operation in its linear region, we can write

$$v_- = v_{IN} = \mathbf{R1/(R1 + R2)}v_{OUT}$$
 or, $\mathbf{v_{OUT} = ((R1 + R2)/R1)v_{IN}}$
- We can derive the same expression by writing



$$v_{OUT} = A(v_+ - v_-) = A\{v_{IN} - [\mathbf{R1/(R1 + R2)}] v_{OUT}\}$$
 and solving for v_{OUT} with $A \gg 1$
 Look at Example 2.1 and plot transfer curve.

The Concept of the Virtual Short

- The op-amp with negative feedback forces the two inputs v_+ and v_- to have the same voltage, even though no current flows into either input.
 - This is sometimes called a “**virtual short**”
 - As long as the op-amp stays in its linear region, the output will change up or down until v_- is almost equal to v_+
 - If v_{IN} is raised, v_{OUT} will increase just enough so that v_- (tapped from the voltage divider) increases to be equal to v_+ ($= v_{IN}$)
 - In v_{IN} is lowered, v_{OUT} lowers just enough to make $v_- = v_+$
 - The negative feedback forces the “virtual short” condition to occur
- Look at Exercise 2.4 and 2.5
- For consideration:
 - What would the op-amp do if the feedback connection were connected to the v_+ input and v_{IN} were connected to the v_- input?
 - Hint: This connection is a positive feedback connection!


Linear Op-amp Operation: Inverting Configuration

Fig. 2.8 (a) Inverting amplifier configuration; (b) block diagram of circuit's operational function.

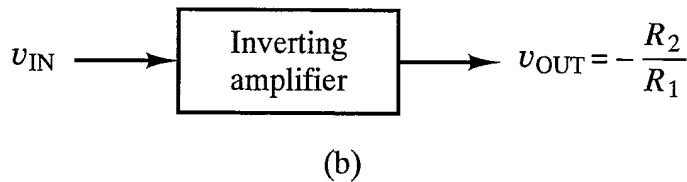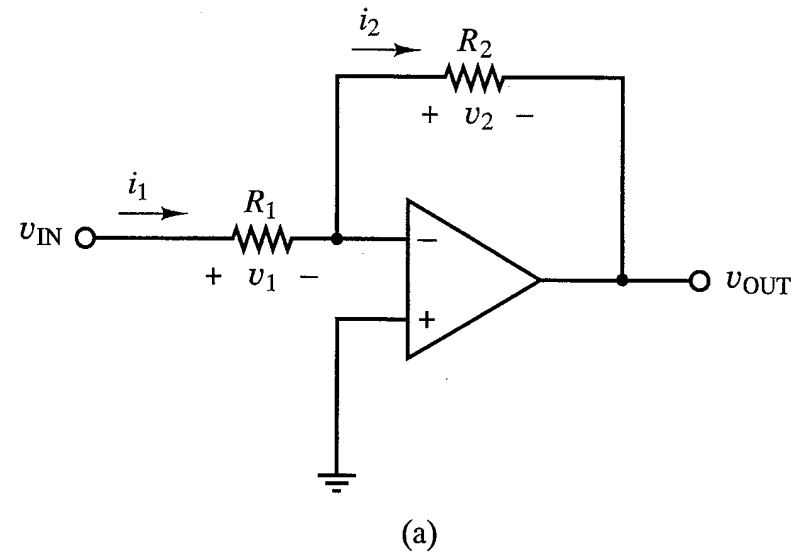

- An op-amp in the inverting configuration (with negative feedback) is shown at the left
 - Feedback is from v_{OUT} to v_- through resistor R_2
 - v_{IN} comes in to the v_- terminal via resistor R_1
 - v_+ is connected to ground
- Since $v_- = v_+ = 0$ and the input current is zero, we can write
 - $i_1 = (v_{IN} - 0)/R_1 = i_2 = (0 - v_{OUT})/R_2$ or,

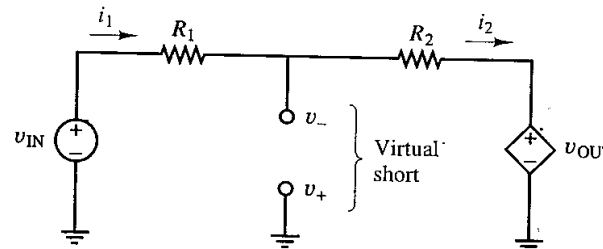
$$v_{OUT} = - (R_2/R_1) v_{IN}$$
- The circuit can be thought of as a resistor divider with a virtual short (as shown below)
 - If the input v_{IN} rises, the output v_{OUT} will fall just enough to hold v_- at the potential of v_+ ($=0$)
 - If the input v_{IN} drops, v_{OUT} will rise just enough to force v_- to be very near 0
- Look at Example 2.2 and Exercises 2.7-2.10




Input Resistance for Inverting and Non-inverting Op-amps

- The non-inverting op-amp configuration of slide 2-4 has an apparent input resistance of infinity, since $i_{IN} = 0$ and $\mathbf{R}_{IN} = \mathbf{v}_{IN}/\mathbf{i}_{IN} = \mathbf{v}_{IN}/0 = \mathbf{infinity}$
- The inverting op-amp configuration, however, has an apparent input resistance of R1
 - since $\mathbf{R}_{IN} = \mathbf{v}_{IN}/\mathbf{i}_{IN} = \mathbf{v}_{IN}/[(\mathbf{v}_{IN} - 0)/\mathbf{R1}] = \mathbf{R1}$

Op-amp Voltage Follower Configuration

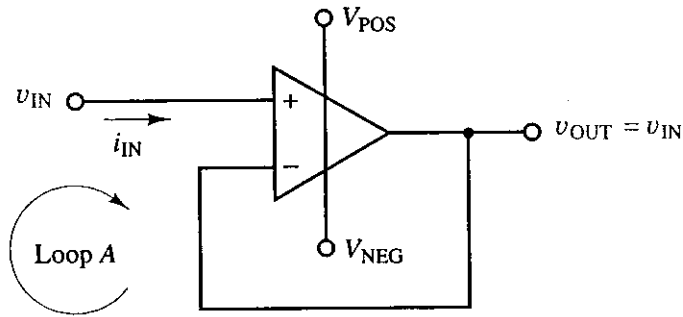


- The op-amp configuration shown at left is a voltage-follower often used as a buffer amplifier
 - Output is connected directly to negative input (negative feedback)
 - Since $v_+ = v_- = v_{IN}$, and $v_{OUT} = v_-$, we can see by inspection that the closed-loop gain $A_o = 1$
 - We can obtain the same result by writing
$$v_{OUT} = A(v_{IN} - v_{OUT}) \quad \text{or}$$
$$v_{OUT}/v_{IN} = A/(1 + A) = 1 \quad \text{for } A \gg 1$$

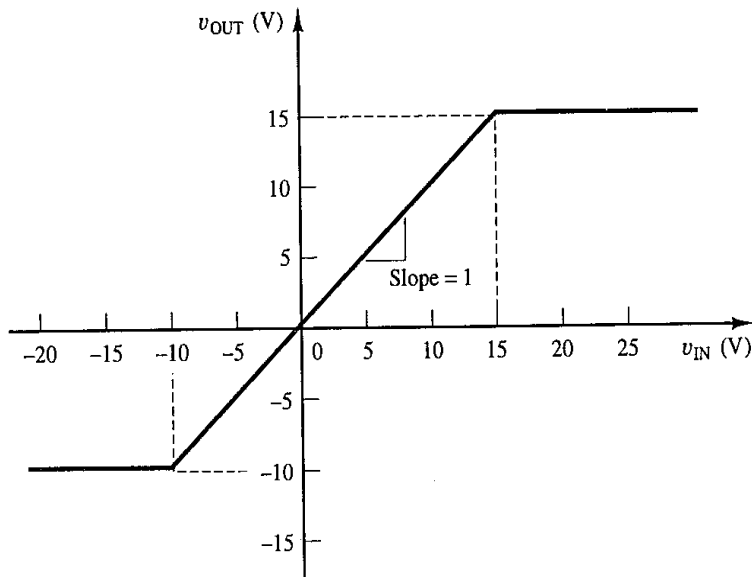

- A typical voltage-follower transfer curve is shown in the left-bottom figure for the case $V_{POS} = +15V$ and $V_{NEG} = -10V$
 - For v_{IN} between -10 and $+15$ volts, $v_{OUT} = v_{IN}$
 - If v_{IN} exceeds $+15V$, the output saturates at V_{POS}
 - If $v_{IN} < -10V$, the output saturates at V_{NEG}
- Since the input current is zero giving zero input power, the voltage follower can provide a large power gain
- Example 2.3 in text.

Op-amp Difference Amplifier

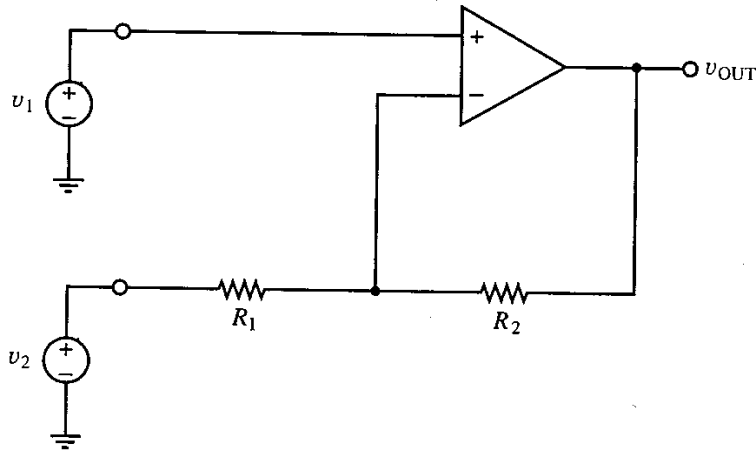


- The “difference amplifier” shown at the left-top combines both the inverting and non-inverting op-amps into one circuit
 - Using superposition of the results from the two previous cases, we can write
 - $v_{OUT} = [(R1 + R2)/R1]v_1 - (R2/R1)v_2$
 - The gain factors for both inputs are different, however


- We can obtain the same gain factors for both v_1 and v_2 by using the modified circuit below
 - Here the attenuation network at v_1 delivers a reduced input $v_+ = v_1(R2/(R1 + R2))$
 - Replacing v_1 in the expression above by the attenuation factor, gives us

$$v_{OUT} = (R2/R1)(v_1 - v_2)$$

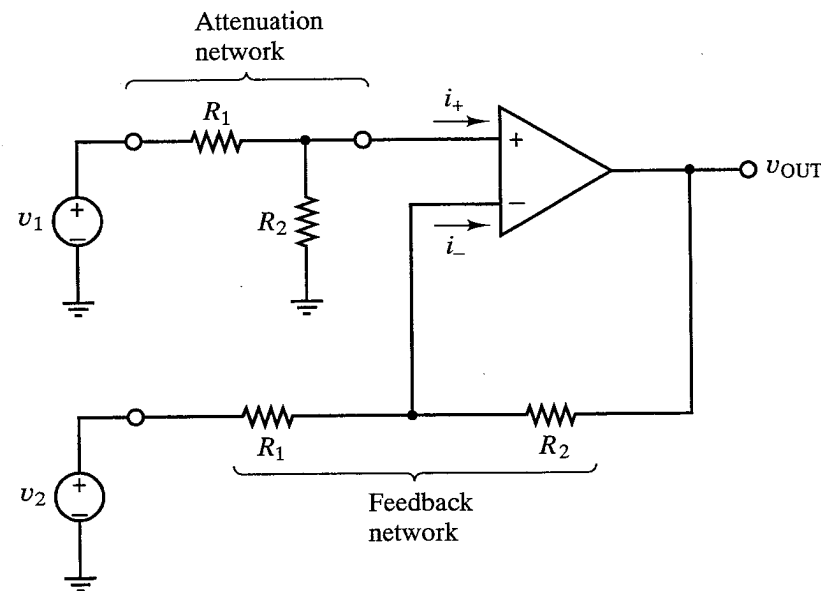- The difference amplifier will work properly if the attenuation network resistors (call them $R3$ & $R4$) are related to the feedback resistors $R1$ & $R2$ by the relation $R3/R4 = R1/R2$ (i.e. same ratio)




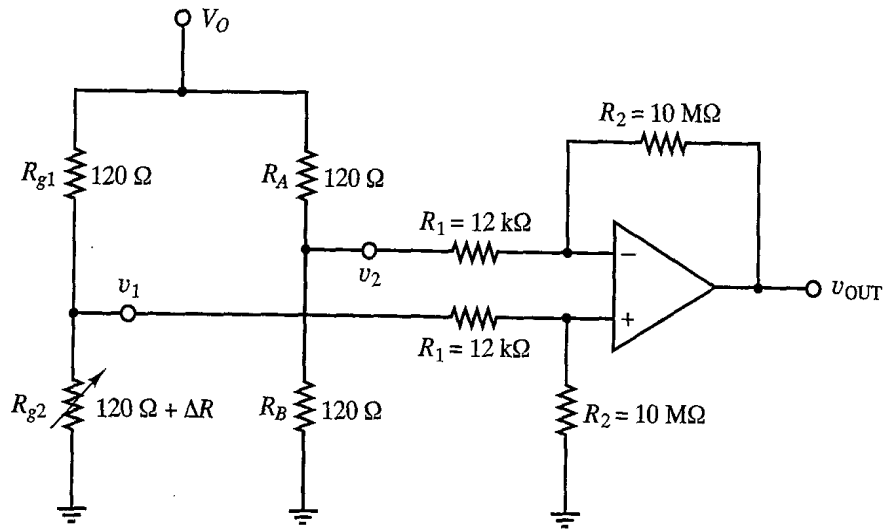Ex. Difference Amplifier with a Resistance Bridge



- The example of Fig's 2.14 and 2.15 in the text shows a difference amplifier used with a bridge circuit and strain gauge to measure strain.
- Operation:
 - The amplifier measures a difference in potential between v_1 and v_2 .
 - By choosing $R_A = R_B = R_g$ (unstressed resistance of R_{g1} and R_{g2}), it is possible to obtain an approx linear relationship between v_{OUT} and ΔL , where ΔL is proportional to the strain across the gauge.
- Design:
 - In order for the bridge to be accurate, the input resistances of the difference op-amp must be large compared to R_A , R_B , & R_g
 - Input resistance at v_1 (with v_2 grounded) is $R_1 + R_2 \approx 10\ \text{Mohm}$
 - Input resistance at v_2 (with v_1 grounded) is just $R_1 = 12\ \text{K}$ due to the v_1 - v_2 virtual short

Instrumentation Amplifier

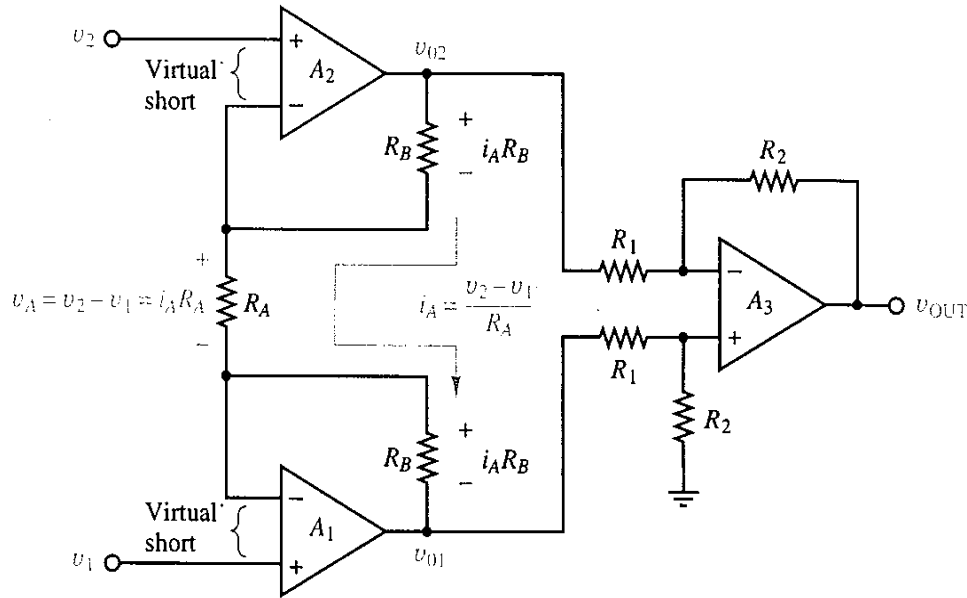

- Some applications, such as an oscilloscope input, require differential amplification with extremely high input resistance
- Such a circuit is shown at the left
 - A3 is a standard difference op-amp with differential gain R_2/R_1
 - A1 and A2 are additional op-amps with extremely high input resistances at v1 and v2 (input currents = 0)


- Differential gain of input section:

- Due to the virtual shorts at the input of A1 and A2, we can write $i_A = (v_2 - v_1) / R_A$
- Also, i_A flows through the two R_B resistors, allowing us to write $v_{02} - v_{01} = i_A (R_A + 2 R_B)$
- Combining these two equations with the gain of the A3 stage, we can obtain

$$v_{OUT} = (R_2/R_1)(1 + [2R_B/R_A])(v_1 - v_2)$$

- By adjusting the resistor R_A , we can adjust the gain of this instrumentation amplifier


Summation Amplifier

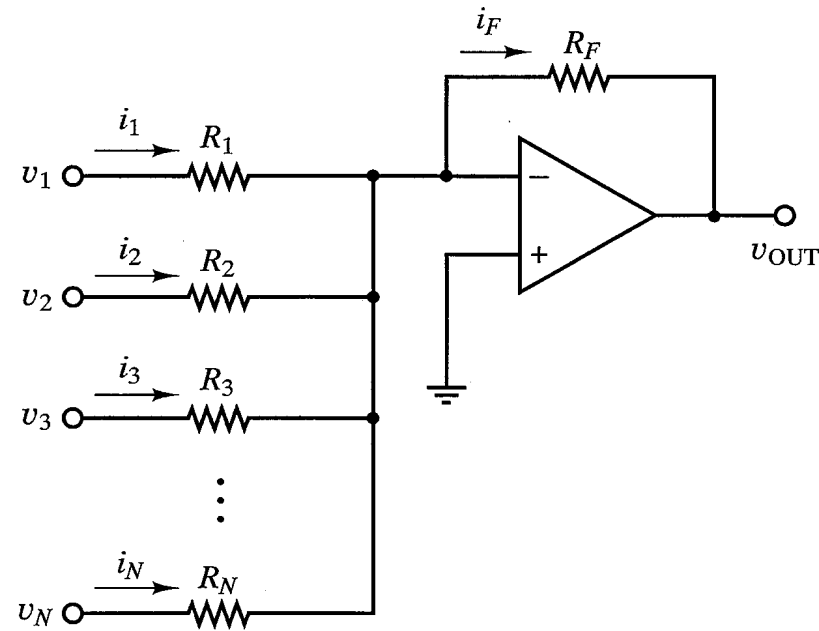

- A summation op-amp (shown at left) can be used to obtain a weighted sum of inputs $v_1 \dots v_N$
 - The gain for any input k is given by R_F/R_k
- If any input goes positive, v_{OUT} goes negative just enough to force the input v_- to zero, due to the virtual short nature of the op-amp
 - Combining all inputs, we have
$$v_{OUT} = -R_F(v_1/R_1 + v_2/R_2 + \dots + v_N/R_N)$$
 - The input resistance for any input k is given by R_k due to the virtual short between v_- and v_+
- Example 2.5 – use as an audio preamp with individual adjustable gain controls
 - Note effect of microphone's internal resistance


Op-amp with T-bridge Feedback Network

- To build an op-amp with high closed-loop gain may require a high value resistor R_2 which may not be easily obtained in integrated circuits due to its large size
- A compromise to eliminate the high value resistor is the op-amp with T-bridge feedback network, shown below
 - R_A and R_B comprise a voltage divider generating node voltage $v_B = v_{OUT} R_B / (R_A + R_B)$, assuming that $R_2 \gg R_A \parallel R_B$
 - Since v_B is now fed back to v_- , an apparent gain $v_B / v_{IN} = -(R_2 / R_1)$ can be written
- Combining these two equations allows us to write $v_{OUT} = - (R_2 / R_1) ([R_A + R_B] / R_B) v_{IN}$
- Fairly large values of closed-loop gain can be realized with this network without using extremely large IC resistors

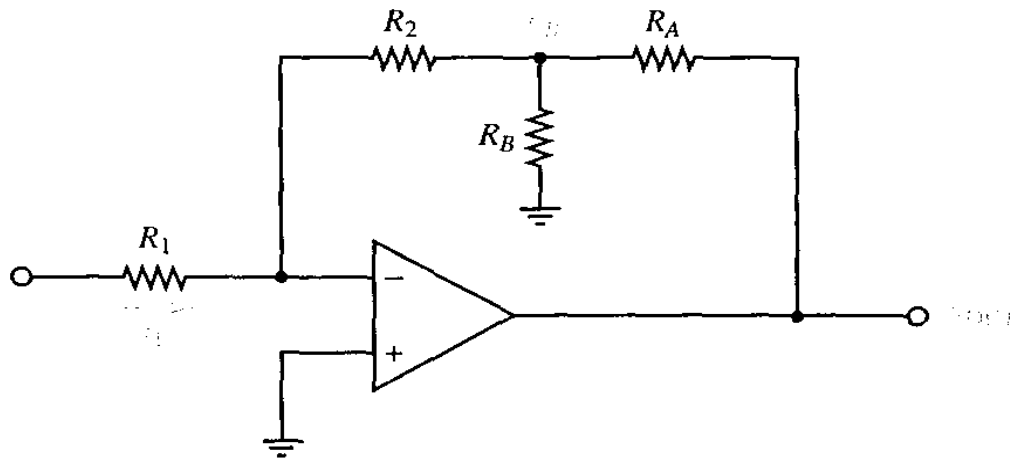


Op-amp Integrator Network

- Shown below is an op-amp integrator network
 - The output will be equal to the integral of the input, as long as the op-amp remains in its linear region
 - Due to the virtual short property of the op-amp input, we can write $i_1 = v_{IN}/R_1$
 - This current i_1 starts charging the capacitor C according to the relation $i_1 = C(dv_C/dt)$
- Since v_- remains at GND, the output drops below GND as C charges and the time derivative of v_{OUT} becomes the negative of the time derivative of v_C
 - since $v_C = 0 - v_{OUT}$
- Combining the above equations, we obtain
 - $dv_{OUT}/dt = -i_1/C = -v_{IN}/R_1C$
- Solving for $v_{OUT}(t)$ and assuming C is initially uncharged, we obtain
 - $v_{OUT}(t) = (-1/R_1C) \int v_{IN} dt$ where the integral is from 0 to t



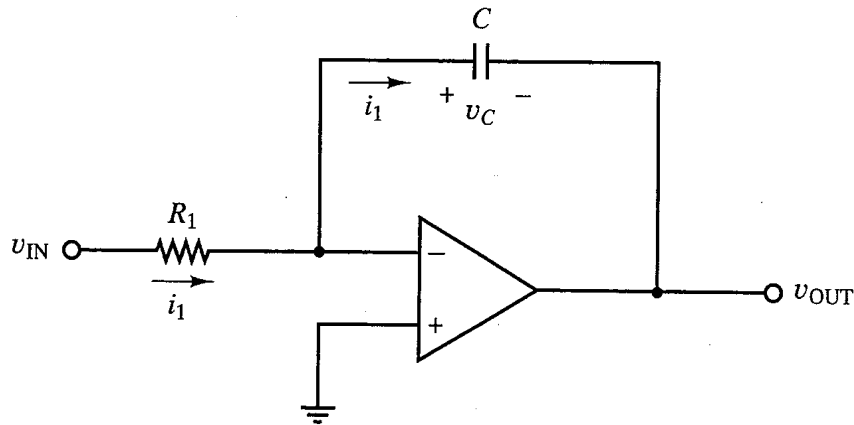


Op-amp Integrator Example

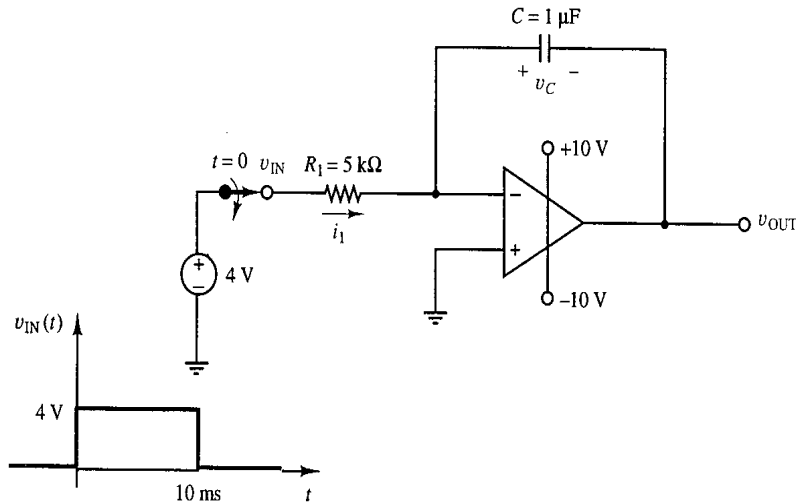- Given an input signal of 4V square wave for 10 ms duration, what is the integrator output versus time for the integrator circuit at the left?




- The current into the capacitor during the square wave is constant at $4\text{V}/5\text{Kohm} = 0.8 \text{ mA}$
- Using the integral expression from the previous chart, the capacitor voltage will increase linearly in time $(1/R_1C) 4t = 0.8t \text{ V/ms}$ during the square wave duration
- The output will therefore reduce linearly in time by $-0.8t \text{ V/ms}$ during the pulse duration, falling from 0 to -8 volts , as shown in the figure at left
- Since at 10 ms the output will be $-8 \text{ V} > V_{\text{NEG}}$, the op-amp will not saturate during the 10 ms input pulse

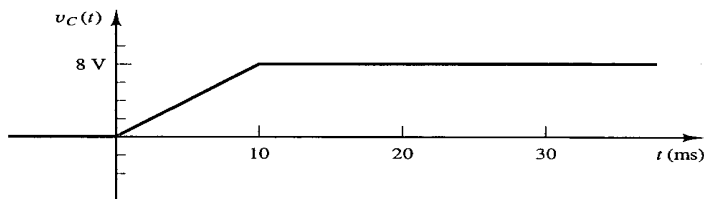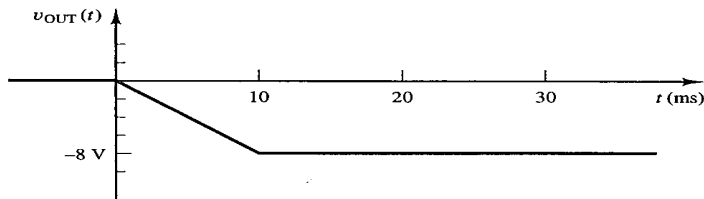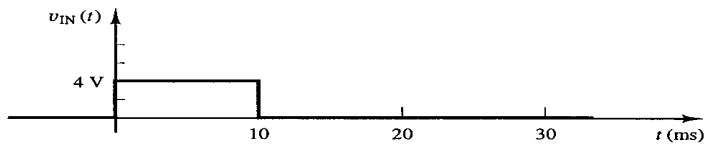



Op-amp Integrator Example with Long Pulse

- Consider a case with an infinitely long 4V pulse
 - The capacitor will continue to charge linearly in time, but will eventually reach 10V which will force v_{OUT} to $-10V (= V_{NEG})$ and saturate the op-amp (at 12.5 ms)
 - After this time, the op-amp will no longer be able to maintain v_- at 0 volts
 - Since v_{OUT} is clamped at $-10V$, the capacitor will continue to charge exponentially with time constant R_1C until $v_- = +4V$
 - During this time the capacitor voltage will be given by
$$v_C(t) = 10 + 4[1 - \exp(t_1 - t)/R_1C]$$
 where $t_1 = 12.5$ ms
 - At $t = t_1$, $v_C = 10$ V and at $t = \text{infinity}$, $v_C = 14$ V
 - The resulting capacitor and output waveforms are shown below.

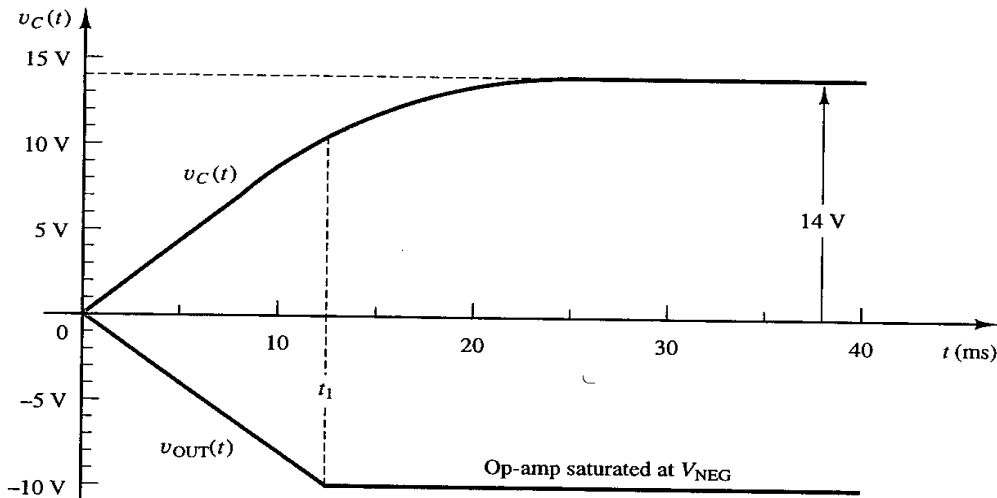



Op-amp as a Differentiator

- The two op-amp configurations shown below perform the function of differentiation
 - The circuit on the left is the complement of the integrator circuit shown on slide 2-14, simply switching the capacitor and resistor
 - The circuit on the right differentiates by replacing the capacitor with an inductor
- For the circuit on the left we can write
 - $i_1 = C(dv_{IN}/dt) = i_2 = (0 - v_{OUT})/R_2$ or
$$v_{OUT} = - R_2 C (dv_{IN}/dt)$$
- Similarly, for the circuit on the right we can obtain
$$v_{OUT} = - (L/R_1) (dv_{IN}/dt)$$
- By nature a differentiator is more susceptible to noise in the input than an integrator, since the slope of the input signal will vary wildly with the introduction of noise spikes.
- Do exercises 2.23 and 2.25.



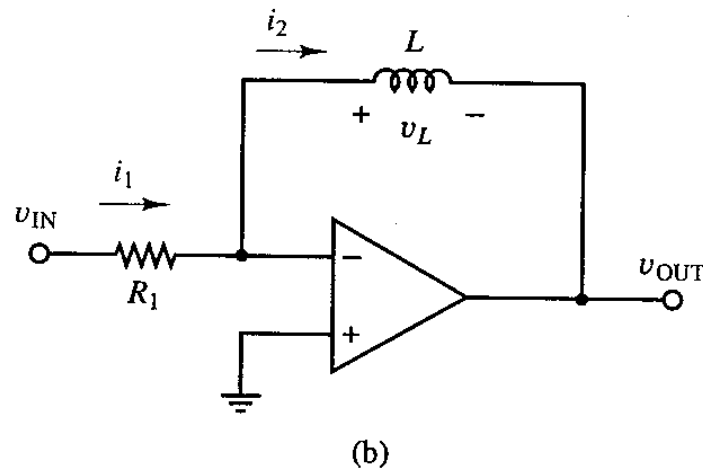
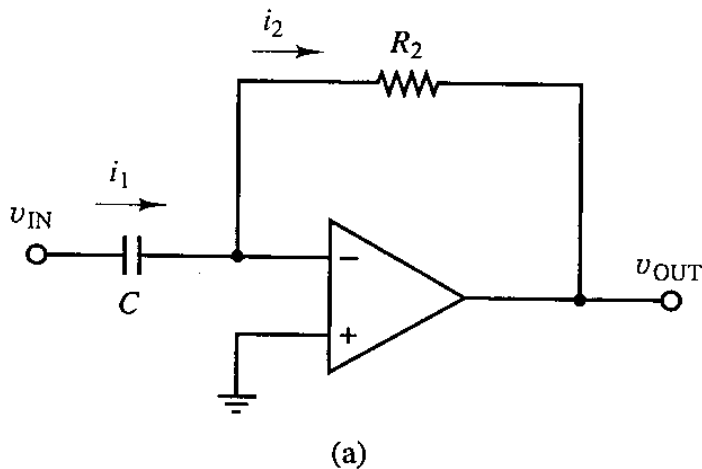


Non-Linear Op-amp Circuits

- Op-amps are sometimes used in non-linear open-loop configurations where the slightest change in v_{IN} will force the op-amp into saturation (V_{POS} or V_{NEG})
 - Such non-linear op-amp uses are often found in signal processing applications
- Two examples of such non-linear operation are shown at the left
 - Left-top is an **open-loop polarity indicator**
 - If v_{IN} is above or below GND by a few mV, v_{OUT} is forced to either positive or negative rail voltage
 - Left-bottom is an **open-loop comparator**
 - If v_{IN} is above or below V_R by a few mV, v_{OUT} is forced to the positive or negative rail voltage

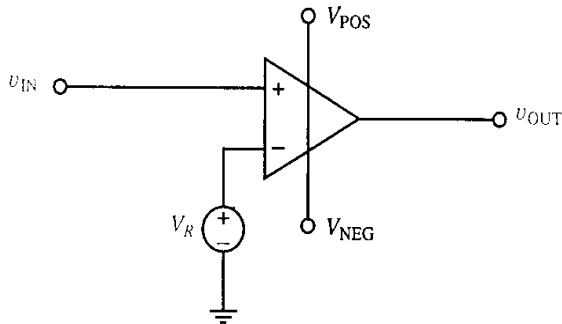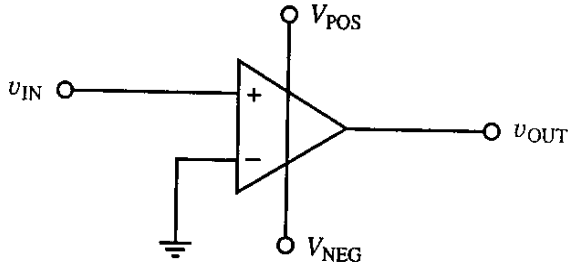


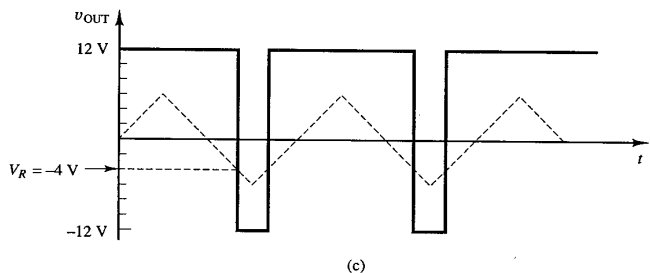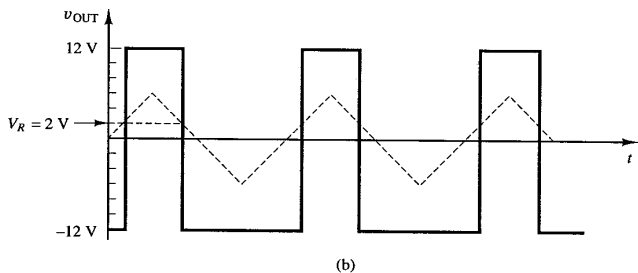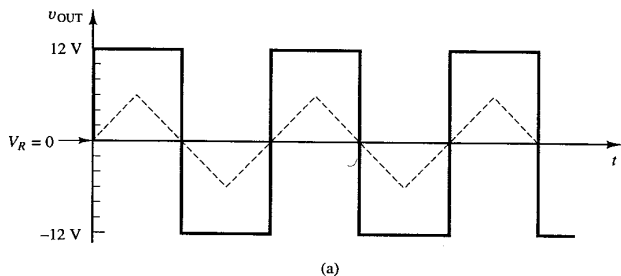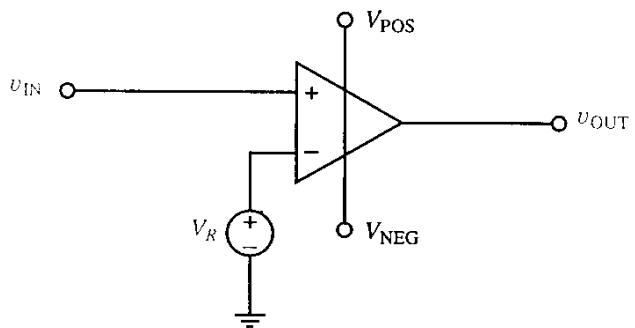Open-Loop Comparator (Example 2.8 in text)




- Given the open-loop comparator shown at the left with $V_{\text{POS}} = +12\text{V}$ and $V_{\text{NEG}} = -12\text{V}$, plot the output waveforms for $V_R = 0$, $+2\text{V}$, and -4V , assuming v_{IN} is a 6V peak triangle wave
- The solution is shown at the left
 - In (a) the output switches symmetrically from VPOS rail to V_{NEG} rail as the input moves above or below GND
 - In (b) the output switches between the rail voltages as the input goes above or below $+2\text{V}$
 - In (c) the output switches between the rail voltages as the input varies above or below -4V
 - The output becomes a pulse generator with adjustable pulse width
- Do Exercise 2.28.


Schmitt Trigger Op-amp Circuit

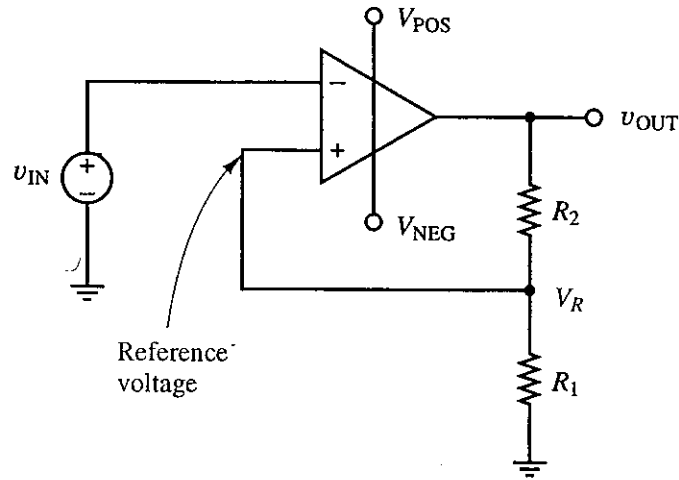


- The open-loop comparator from the previous two slides is very susceptible to noise on the input
 - Noise may cause it to jump erratically from + rail to – rail voltages
- The Schmitt Trigger circuit (at the left) solves this problem by using positive feedback
 - It is a comparator circuit in which the reference voltage is derived from a divided fraction of the output voltage, and fed back as positive feedback.
 - The output is forced to either V_{POS} or V_{NEG} when the input exceeds the magnitude of the reference voltage
 - The circuit will remember its state even if the input comes back to zero (has memory)
- The transfer characteristic of the Schmitt Trigger is shown at the left
 - Note that the circuit functions as an inverter with hysteresis
 - Switches from + to – rail when $v_{IN} > V_{POS} \frac{R1}{R1 + R2}$
 - Switches from – to + rail when $v_{IN} < V_{NEG} \frac{R1}{R1 + R2}$

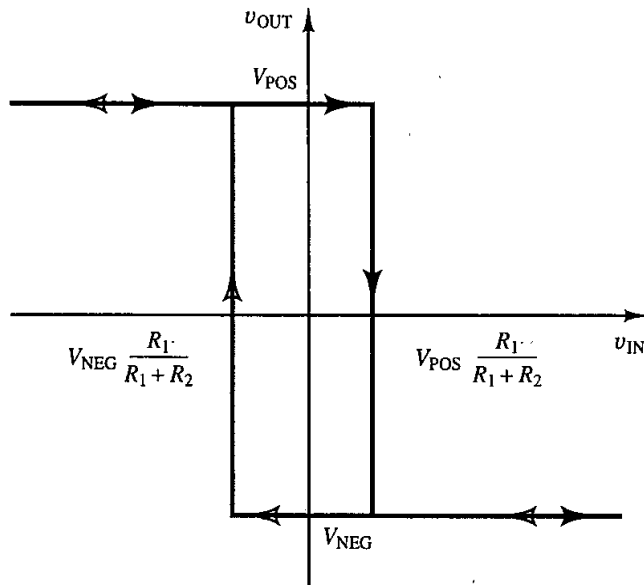

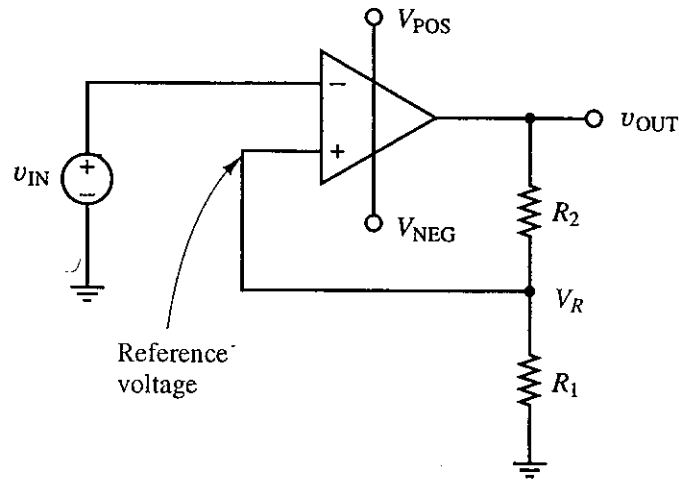Schmitt Trigger Op-amp Example (2.9 in text)




- Assume that for the Schmitt trigger circuit shown at the left, $V_{POS}/NEG = +/- 12$ volts, $R1 = R2$, and v_{IN} is a 10V peak triangular signal. What is the resulting output waveform?
- Answer:
 - The output will switch between +12 and –12 volts
 - The switch to V_{NEG} occurs when v_{IN} exceeds $V_{POS}(R1/(R1 + R2)) = +6$ volts
 - The switch to V_{POS} occurs when v_{IN} drops below $V_{NEG}(R1/(R1 + R2)) = -6$ volts
 - See waveforms at left
- Consider the case where we start out the Schmitt Trigger circuit with $v_{IN} = 0$ and $v_{OUT} = 0$ (a quasi-stable solution point for the circuit)
 - However, any small noise spike on the input will push the output either in the + or – direction, causing v_{OUT} to also go in the same direction, which will cause the output to move further in the same direction, etc. until the output has become either V_{POS} or V_{NEG} .

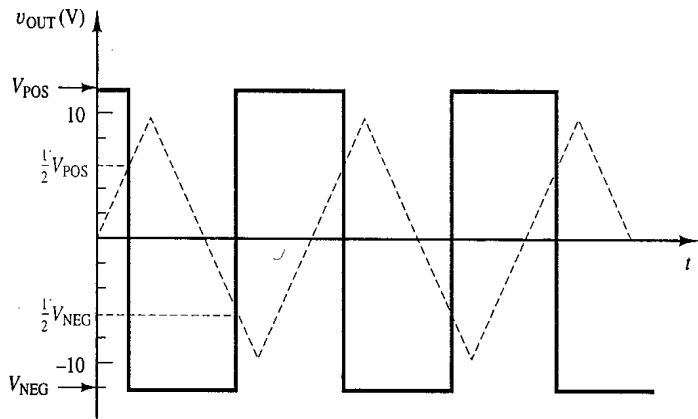

Non-Ideal Properties of Op-amps: Output Saturation and Input-Offset Voltage

Output Saturation Voltage

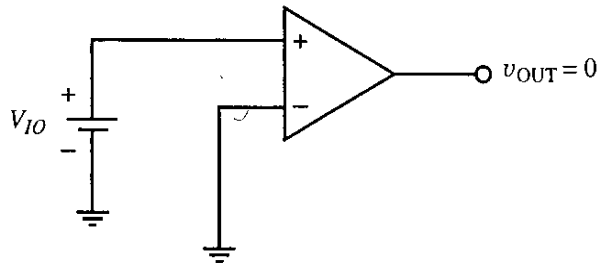
- Although we have been assuming the op-amp will saturate at the supply voltages V_{POS} and V_{NEG} , in actual practice an op-amp circuit will saturate at somewhat lower than V_{POS} and higher than V_{NEG} , due to internal voltage drops in the design
 - Emitter-follower output stage (BJT design) will drop a V_{BE}
 - CMOS design will have a similar drop



Input-Offset Voltage

- We have been assuming $v_+ = v_-$ when $v_{OUT} = 0$. In actual practice, however, there is usually a small input (or output) dc offset voltage in order to force v_{OUT} to 0, under open-loop operation.
 - The input-offset voltage (labeled V_{IO} in the figure at the left) can be positive or negative and is usually small (anywhere from 1 μ V to 10 mV)

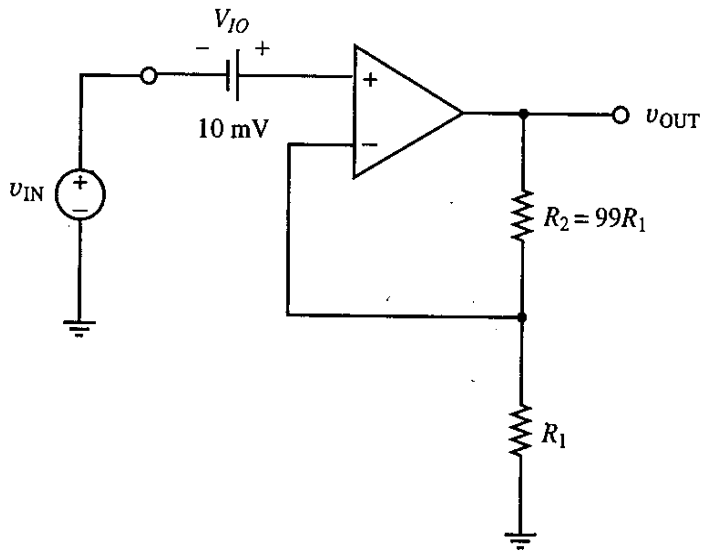Input-Offset Voltage Effect on Output Voltage



- To examine the effect input-offset voltage has on the output voltage, consider the non-inverting op-amp
 - The gain of the op-amp is $(R_1 + R_2)/R_1 = 100$
 - Assume the input voltage is modeled adequately by a source $V_{IO} = +/- 10 \text{ mV}$
 - Then, we can write that the output voltage is given by


$$v_{OUT} = (v_{IN} + V_{IO})(R_1 + R_2)/R_1$$

$$= 100 v_{IN} +/- 1 \text{ volt}$$
 - Thus, a 10 mV input-offset causes a 1V offset in v_{OUT}
- Exercise 2.32: Show that the above equation applies even if V_{IO} is placed in series with the v- input, instead of the v+ input.
 - Using the virtual short condition, we can write


$$v_{OUT}[R_1/(R_1 + R_2)] + V_{IO} = v_{IN} \quad \text{or}$$

$$v_{OUT} = (R_1 + R_2)/R_1(v_{IN} + V_{IO}) \rightarrow \text{same as above!}$$
- Exercise 2.33: What is the output of an inverting op-amp if the effect of input offset is considered?
 - Based on the inverting op-amp circuit of slide 2-6, we can write $i_1 = (v_{IN} - V_{IO})/R_1 = i_2 = (V_{IO} - v_{OUT})/R_2$
 - or, $v_{OUT} = - (R_2/R_1) v_{IN} + V_{IO} (R_1 + R_2)/R_1$

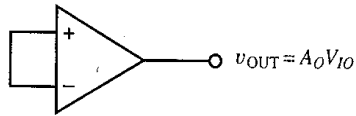Output-Offset Voltage and Nulling Out Offset




(a)

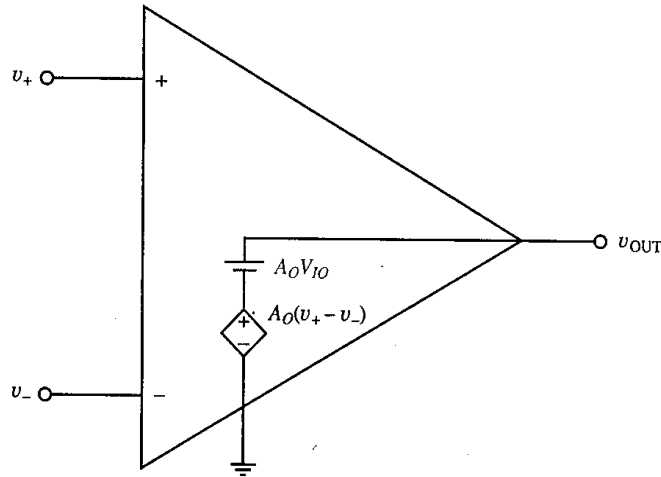

(b)

- A parameter called the **output-offset voltage** may be used to represent the internal imbalance of an op-amp, rather than the input-offset voltage
 - The output-offset voltage is defined as the measured output voltage when the input terminals are shorted together, as shown at the left-top fig.
 - The output-offset voltage may be modeled by placing a voltage source $A_0 V_{IO}$ in series with the output voltage source $A_0(v_+ - v_-)$
 - Consequently, the output-offset voltage is essentially the input-offset voltage multiplied by the open loop gain.
 - Do exercise 2.34
- How can we correct for offset voltage?
 - Some op-amps provide two terminals (offset-null terminals) for adjusting out the offset voltage
 - A potentiometer is connected across the offset null terminals with the V_{NEG} supply voltage connected to the adjustable center tap
 - If the op-amp does not have an internal null adjustment provision, an external adjustment similar to that shown in Example 2.11 can be provided.
- Look at Exercise 2.36 (error in text)


Effect of Non-zero Input Bias Currents

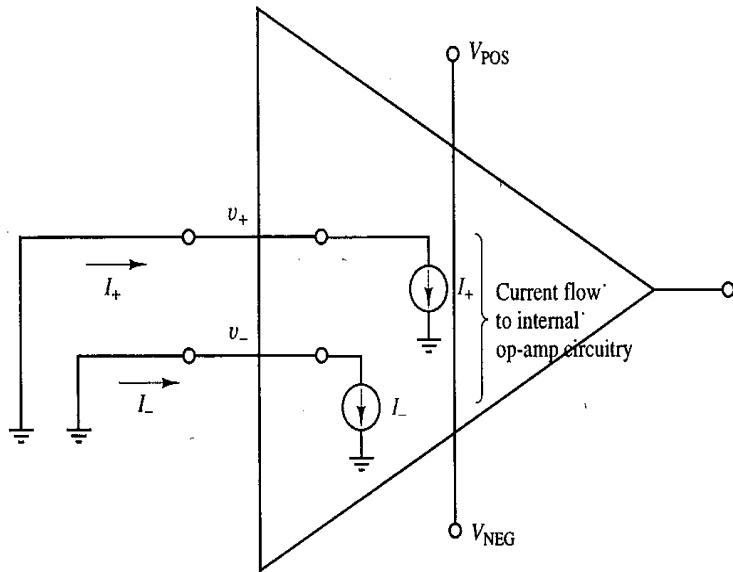

- In practice op-amps do not actually have zero input currents, but rather have very small input currents labeled I_+ and I_- in the figure at the left
 - Modeled as internal current sources inside op-amp
 - I_+ and I_- are both the same polarity
 - e.g. if the input transistors are NPN bipolar devices, positive I_+ and I_- are required to provide base current
 - In order to allow for slightly different values of I_+ and I_- , we define the term I_{BIAS} as the average of I_+ and I_-

$$I_{BIAS} = \frac{1}{2} (I_+ + I_-)$$

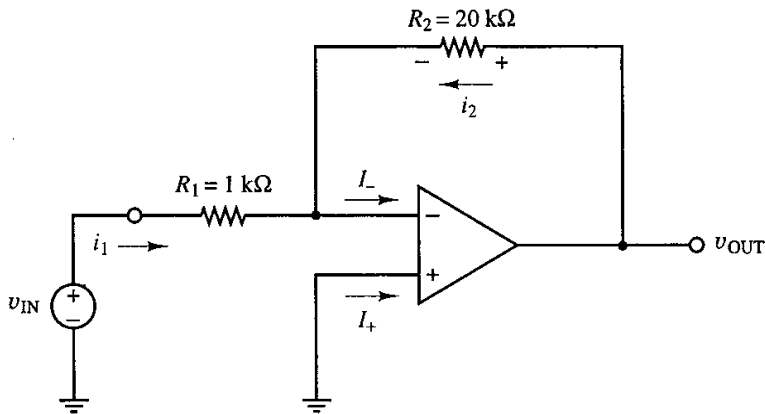
- Example: Given the op-amp shown in the bottom left figure, derive an expression for v_{OUT} that includes the effect of input bias currents



- Assume $I_+ = I_- = 100 \text{ nA}$
- Using the virtual short condition and KCL, we can write $v_{IN}/R_1 = I_- + (0 - v_{OUT})/R_2$ or

$$v_{OUT} = - (R_2/R_1)v_{IN} + I_-R_2$$
- Plugging in values gives $v_{OUT} = - 20 v_{IN} + 2 \text{ mV}$
- Do exercise 2.38, p. 77

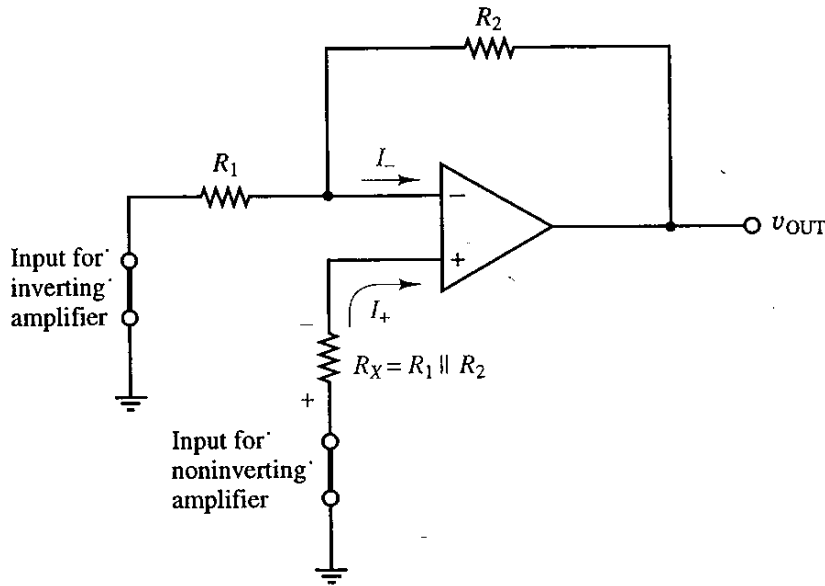Correcting for Non-zero Input Bias Current




- The effect of non-zero input bias current can be zero'ed out by inserting a resistor R_x in series with the V_+ input terminal (as shown)
 - This same correction works for both inverting and non-inverting op-amps
 - We choose R_x such that the dc component on the output caused by I_+ exactly cancels the dc component on v_{OUT} caused by I_-
 - One can use either KCL (Kirchhoff's Current Law) or superposition to show that choosing $R_x = R_1 \parallel R_2$ completely cancels out the dc effect of non-zero input bias current
- KCL Method (inverting op-amp at left)
 - v_{IN} is applied to R_1 and R_x is grounded
 - $v_- = v_+ = 0 - I_+ R_x$ due to virtual short
 - Apply KCL to v_+ input:

$$(v_{IN} - v_-)/R_1 = I_- + (v_- - v_{OUT})/R_2$$
 - Solve for v_{OUT} and substitute $-I_+ R_x$ for v_-

$$v_{OUT} = - (R_2/R_1) v_{IN} + I_- R_2 - I_+ R_x (R_1 + R_2)/R_1$$
 - Setting the dc bias terms equal yields

$$R_x = R_1 \parallel R_2 = R_1 R_2 / (R_1 + R_2)$$

Input Offset Current Definition

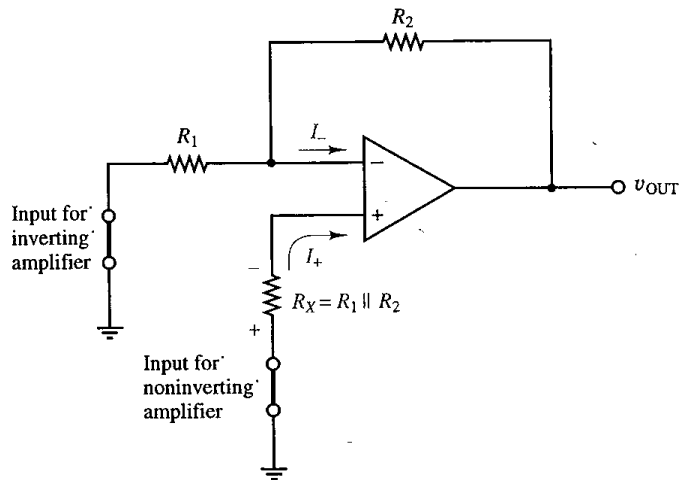

- Non-zero input bias currents I_+ and I_- may not always be equal (some opamps)
 - Variation in bipolar transistor beta may cause base currents to non-track, or perhaps there are circuit design issues causing non equal offset I
- We define a parameter “input offset current”

$$I_{IO} = I_+ - I_-$$
 - Typical values of I_{IO} are 5-10% (of I_-) although it can be as high as 50%
- Example 2.13 based on figure at left
 - $R_1 = 1K$, $R_2 = 20K$ ohms
 - Assuming $I_{bias} = 1 \mu A$ and $I_{IO} = 100 \text{ nA}$, find I_+ , I_- , and the effect of I_{IO} on v_{out}
 - Since $(I_+ + I_-)/2 = 1 \mu A$ and $I_+ - I_- = 0.1 \mu A$, we can solve for $I_+ = 1.05 \mu A$ and $I_- = 0.95 \mu A$
 - Using the expression for V_{out} from slide 2-26 with $V_{in} = 0$ and $R_X = R_1 \parallel R_2$ gives us
 - $v_{OUT} = R_2 (I_- - I_+) = -I_{IO} R_2 = -2 \text{ mV}$
- Do Exercise 2.40


Slew Rate Limitation in an Op-amp

- A real op-amp is limited in its ability to respond instantaneously to an input signal with a high rate of change of its input voltage. This limitation is called the **slew rate**, referring to the maximum rate at which the output can be “slewed”.
 - Typical slew rates may be between $1\text{--}10\text{ V}/\mu\text{s} = 1\text{E}6 - 1\text{E}7\text{ V/s}$
 - Max slew rate is a function of the device performance of the op-amp components & design
 - If the input is driven above the slew rate limit, the output will exhibit non-linear distortion
- Slew rate limitation behavior: (Example 2.14):
 - Assume an inverting op-amp with a gain of -10 has a max slew rate of $1\text{ V}/\mu\text{s}$ and is driven by a sinusoidal input with a peak of 1 V . At what input frequency will the output start to show slew rate limitation?
 - Output has a peak of 10 volts since gain is -10 and input peak is 1 volt
 - If the input is given by $v_{\text{IN}} = V_o \sin \omega t$, the max slope will occur at $t=0$ and will be given by
$$d(V_o \sin \omega t)/dt |_{(t=0)} = \omega V_o = 2\pi f V_o$$
 - The max frequency is therefore given by
$$f_{\text{max}} = \text{slew rate}/2\pi V_o = 1\text{E}6\text{ V/s} / 2\pi 10\text{V} = \sim 16\text{ kHz}$$
 - Note: This surprisingly low max frequency is directly proportional to the slew rate limit spec and inversely proportional to the peak output voltage!

Slew Rate Limitation in an Op-amp


Exceeding the slew rate limitation (Example 2.14b):

- If the inverting op-amp from 2.14a (with gain = -10 and slew rate = $1 \text{ V}/\mu\text{s}$) is driven by a 16 kHz sinusoidal input with a peak of 1.5V , what is the effect on the output waveform?
 - Since we are now exceeding the slew rate limit, the output will be distorted
 - Let $v_{\text{OUT}} = -V_o \cos \omega t$ (for visual simplicity) where $V_o = 10 \times 1.5\text{V} = 15\text{V}$
 - Then $dv_{\text{OUT}}/dt = \omega V_o \sin \omega t$
 - Above some $t = t_1$ the slew rate will limit the output response
- $t_1 = (1/\omega) \sin^{-1}(\text{slew rate}/\omega V_o) = (1/2\pi \times 16 \text{ kHz}) \sin^{-1}(1\text{E}6/2\pi \times 16 \text{ kHz} \times 15\text{V}) = 7.2 \mu\text{s}$
- The resulting waveform is shown below. At t_1 the slew-limited output can't keep up with the input until it catches up at t_2 , when the cycle starts all over again.

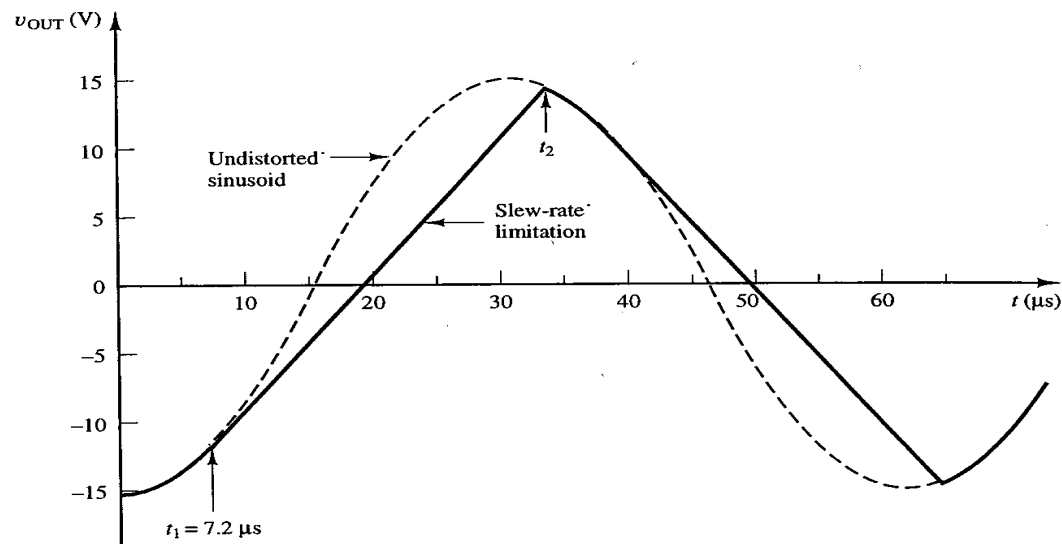


Frequency Response of an Op-amp

- An open-loop op-amp has a constant gain A_o only at low frequencies, and a continuously reducing gain at higher frequencies due to internal device and circuit inherent limits.
 - For a single dominant pole at freq f_p , the frequency-dependent gain $A(j\omega)$ can be written as
$$\mathbf{A(j\omega) = A_o/[1 + j\omega/\omega_p] = A_o/[1 + jf/ f_p]}$$
 where $\omega_p = 2\pi f_p$
 - the gain rolls off at 20dB/decade for frequencies above f_p , as shown below
- An op-amp may have additional higher frequency poles, as well, but is often described over a large frequency range by the dominant pole (as assumed in the figure below)
- The unity gain frequency f_o is defined as the frequency where the gain = 1
 - For the single dominant pole situation assumed in the figure below, f_o can be found by extrapolating the 20 dB/decade roll-off to the point where the gain is unity.

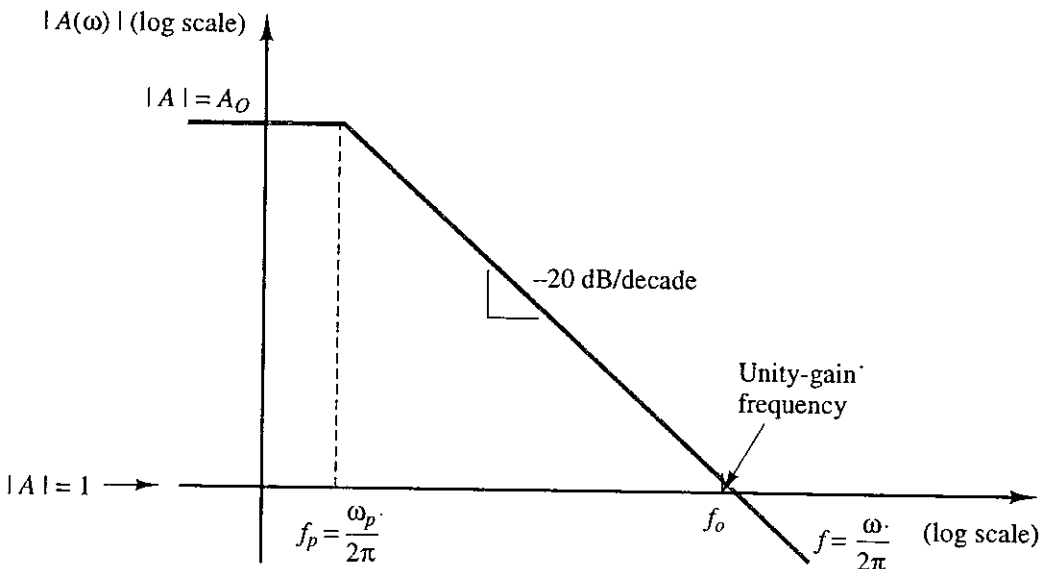

Frequency-Dependent Closed-Loop Gain

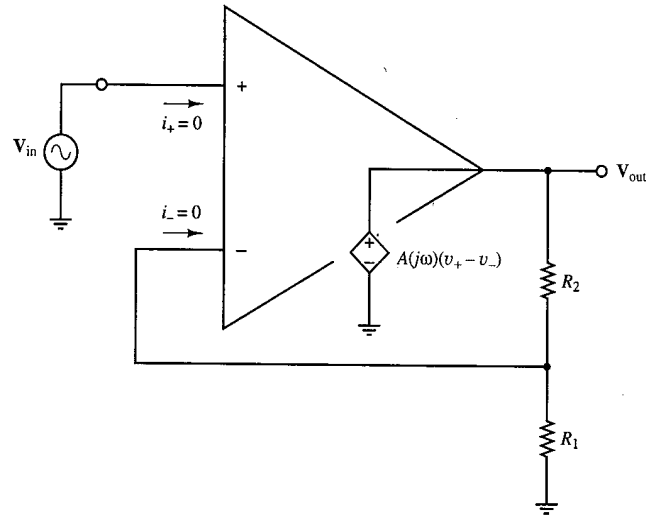

- The effect of the frequency-dependent open-loop gain on the closed-loop gain can easily be found by deriving $v_{OUT}(j\omega)$ as a function of the open-loop gain $A(j\omega)$ in the op-amp configuration shown at the left

$$v_{OUT} = A(j\omega) (v_+ - v_-)$$

$$= A(j\omega) [v_{IN} - v_{OUT}(R1/(R1 + R2))], \text{ or}$$

$$v_{OUT} = A(j\omega)/[1 + A(j\omega)\beta] \quad \text{where}$$


$\beta = R1 / (R1 + R2)$ is the closed-loop feedback function

- Substituting $A(j\omega)$ into the above equation gives us the complete frequency dependent result for the closed loop gain


$$v_{OUT}/v_{IN} = A_o/[1 + A_o\beta + j\omega/\omega_p]$$

$$= [A_o/(1 + A_o\beta)]/[1 + j\omega/\omega_p(1 + A_o\beta)]$$

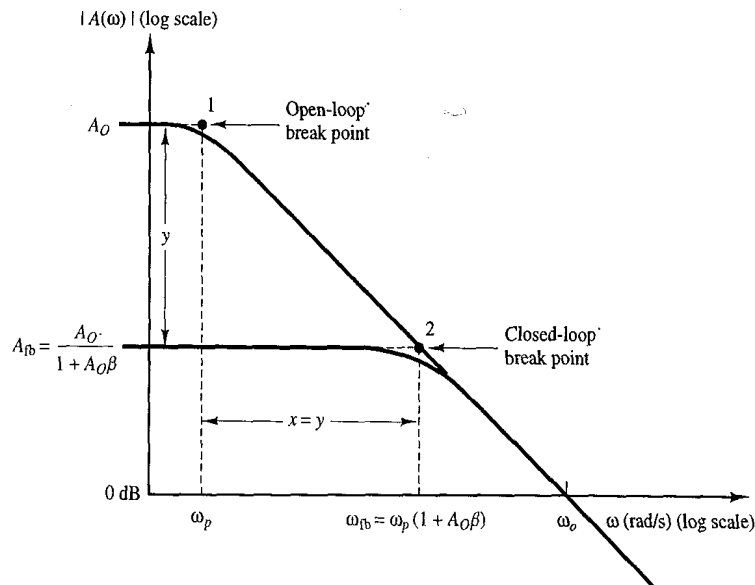- The dc gain is given by
 - $A_o/(1 + A_o\beta) = \sim 1/\beta = (R1 + R2)/R1$
- The closed-loop response is seen to contain a single pole at $\omega_{fb} = \omega_p(1 + A_o\beta) \gg \omega_p$
 - Closed-loop BW = $\sim A_o\beta$ x open-loop BW**



Gain-Bandwidth Product

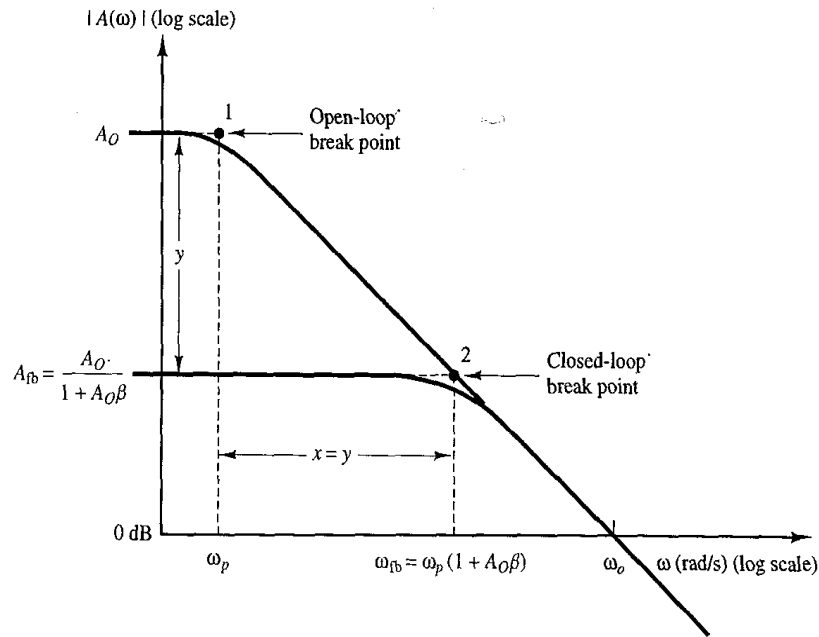

- Multiplication of the closed-loop BW by the closed-loop gain gives us

$$[A_o/(1+A_o\beta)]\omega_{fb} = [A_o/(1+A_o\beta)]\omega_p(1+A_o\beta) = A_o\omega_p$$
 – which is the open-loop gain-BW product
- For the assumption of a single dominant pole and very high A_o , the gain-bandwidth product is a constant
- Unity-gain frequency $\omega_o (= 2\pi f_o)$ is the freq where the op-amp response extrapolates to a gain of 1
 - we can show that $\omega_o = A_o\omega_p$ (for a system with a single dominant pole)

Op-amp Output Current Limit:

- A typical op-amp contains circuitry to limit the output current to a specified maximum in order to protect the output stage from damage
 - If a low value load impedance is utilized, the output current limit may be reached before the output saturates at the rail voltage, forcing the op-amp to lower gain
 - See Example 2.15

Nonlinear Op-Amp Circuits

- Most typical applications require op amp and its components to act linearly
 - I-V characteristics of passive devices such as resistors, capacitors should be described by linear equation (Ohm's Law)
 - For op amp, linear operation means input and output voltages are related by a constant proportionality (A_v should be constant)
- Some application require op amps to behave in nonlinear manner (logarithmic and antilogarithmic amplifiers)


Logarithmic Amplifier

- Output voltage is proportional to the logarithm of input voltage
- A device that behaves nonlinearly (logarithmically) should be used to control gain of op amp
 - Semiconductor diode
- Forward transfer characteristics of silicon diodes are closely described by Shockley's equation

$$I_F = I_S e^{(V_F/\eta V_T)}$$

- I_S is diode saturation (leakage) current
- e is base of natural logarithms ($e = 2.71828$)
- V_F is forward voltage drop across diode
- V_T is thermal equivalent voltage for diode (26 mV at 20°C)
- η is emission coefficient or ideality factor (2 for currents of same magnitude as I_S to 1 for higher values of I_F)



Basic Log Amp operation

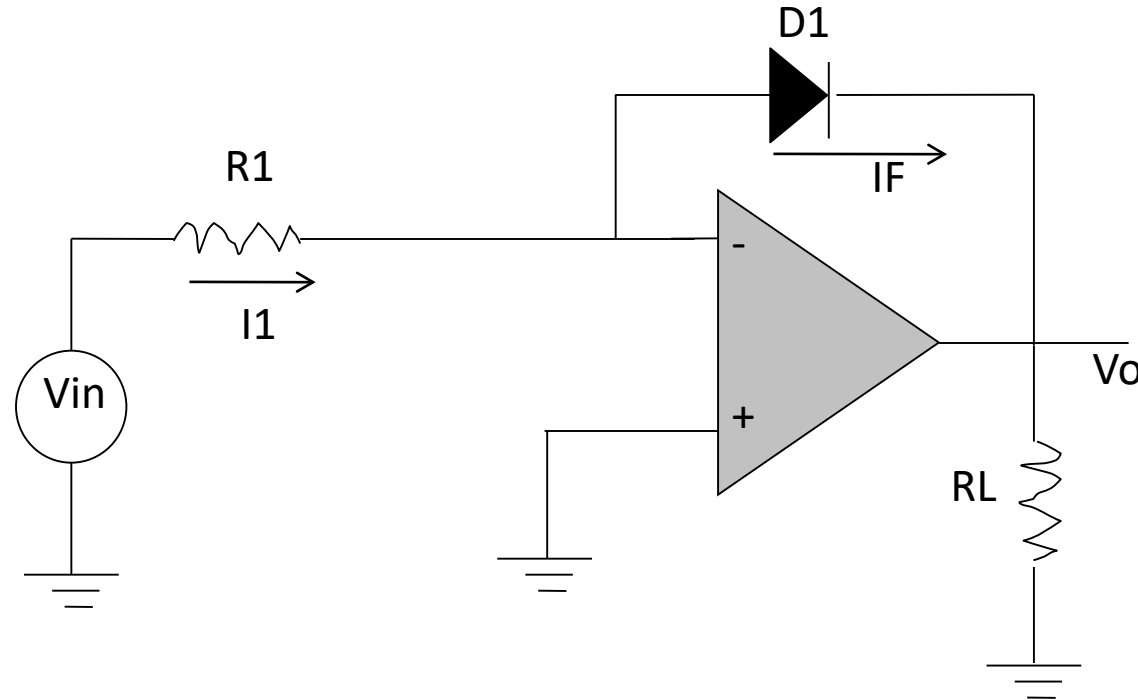


- $I1 = V_{in}/R1$
- $I_F = - I1$
- $I_F = - V_{in}/R1$
- $V_o = -V_F = -\eta V_T \ln(I_F/I_S)$
- $V_o = -\eta V_T \ln[V_{in}/(R1 I_S)]$
- $r_D = 26 \text{ mV} / I_F$
- $I_F < 1 \text{ mA}$ (log amps)
- At higher current levels ($I_F > 1 \text{ mA}$) diodes begin to behave somewhat linearly

Logarithmic Amplifier

- Linear graph: voltage gain is very high for low input voltages and very low for high input voltages
- Semilogarithmic graph: straight line proves logarithmic nature of amplifier's transfer characteristic
- Transfer characteristics of log amps are usually expressed in terms of slope of V_o versus V_{in} plot in millivolts per decade
- η affects slope of transfer curve; I_S determines the y intercept

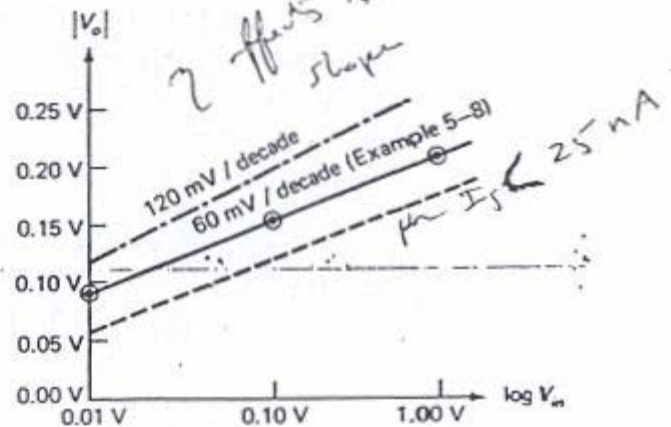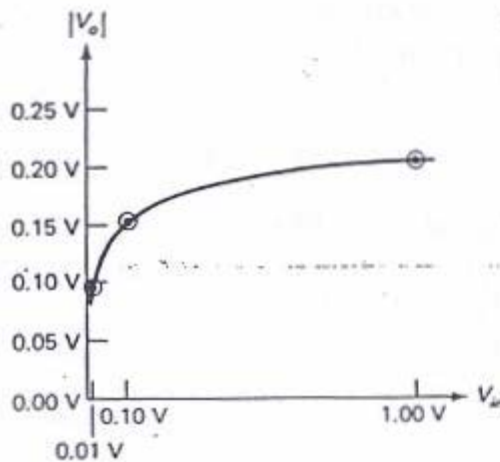

Additional Log Amp Variations

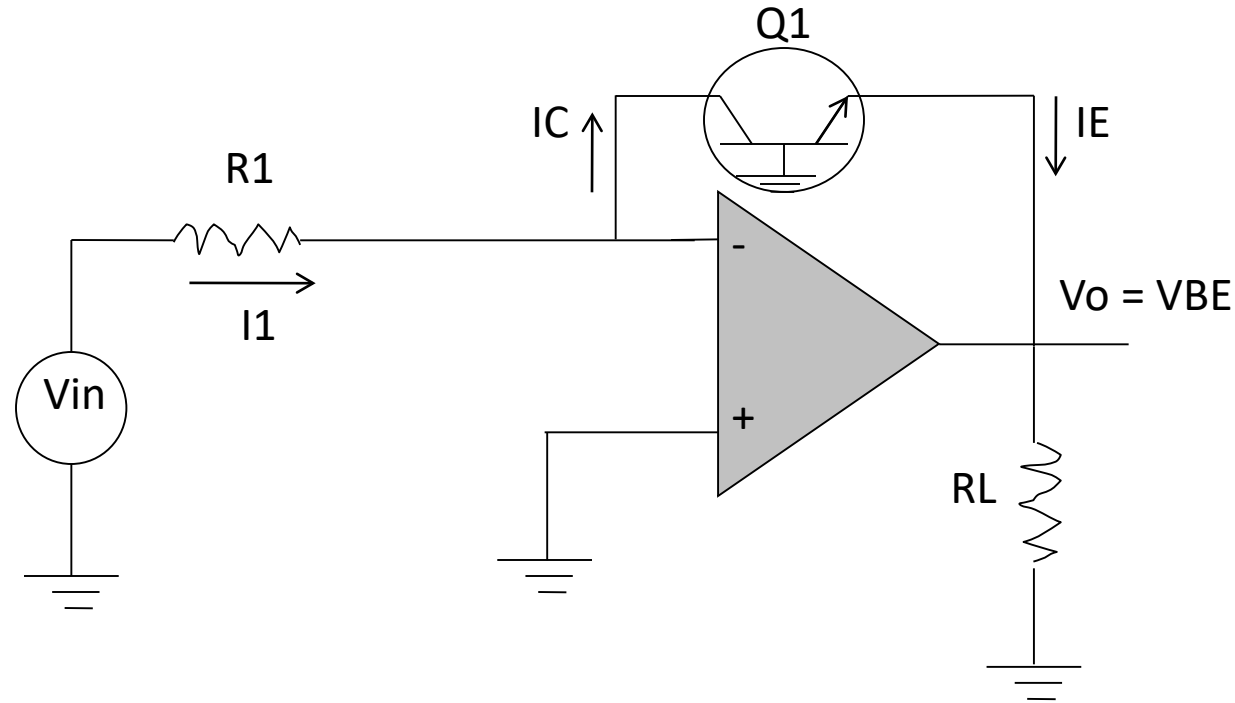

$$I_C = I_{ESe} (V_{BE}/V_T)$$



- I_{ES} is emitter saturation current
- V_{BE} is drop across base-emitter junction

- Often a transistor is used as logging element in log amp (transdiode configuration)
- Transistor logging elements allow operation of log amp over wider current ranges (greater dynamic range)

Antilogarithmic Amplifier

- Output of an antilog amp is proportional to the antilog of the input voltage
- with diode logging element
 - $V_0 = -R_F I_S e^{(V_{in}/V_T)}$
- With transdiode logging element
 - $V_0 = -R_F I_{ES} e^{(V_{in}/V_T)}$
- As with log amp, it is necessary to know saturation currents and to tightly control junction temperature

Antilogarithmic Amplifier

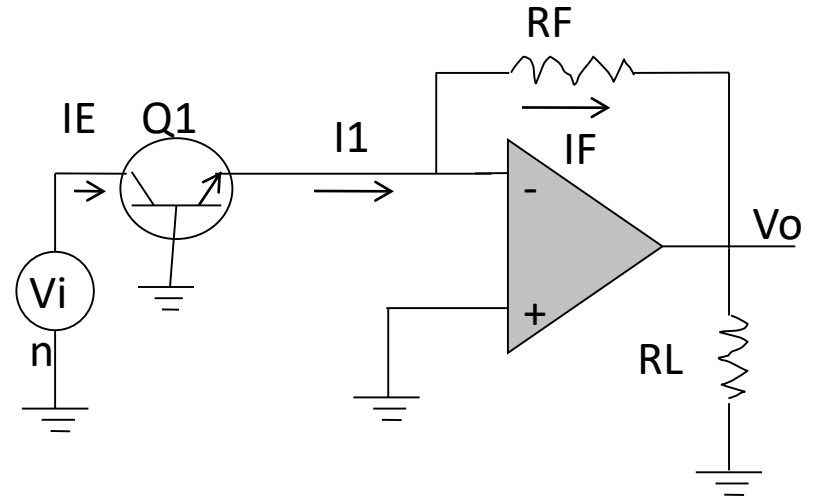
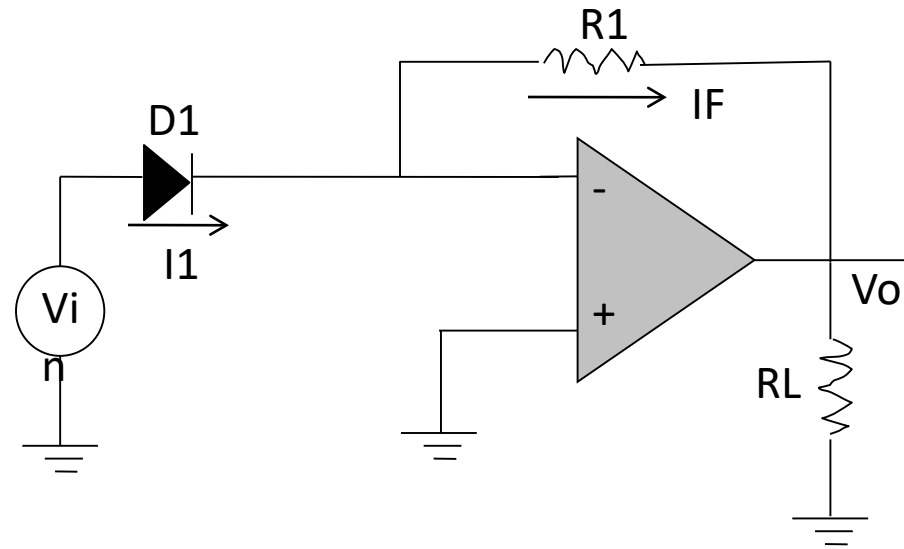


$$(\alpha = 1) I_1 = I_C = I_E$$

Logarithmic Amplifier Applications


- Logarithmic amplifiers are used in several areas
 - Log and antilog amps to form analog multipliers
 - Analog signal processing
- Analog Multipliers
 - $\ln xy = \ln x + \ln y$
 - $\ln (x/y) = \ln x - \ln y$

Analog Multipliers

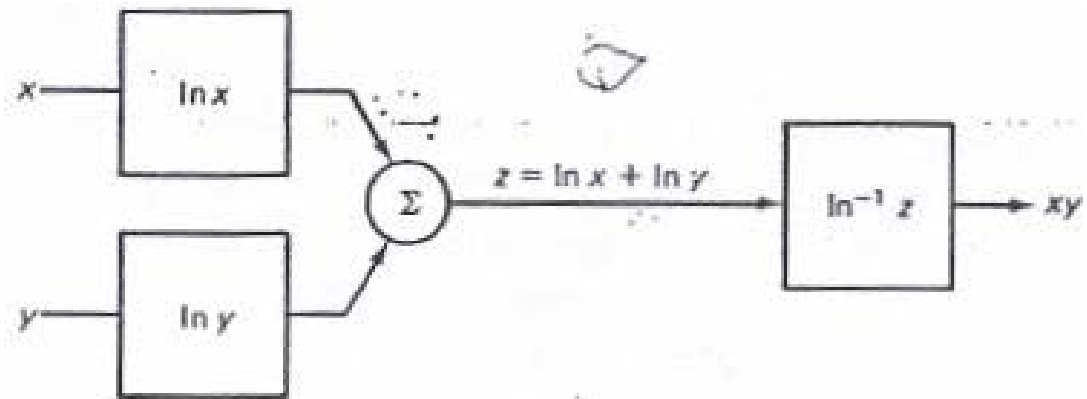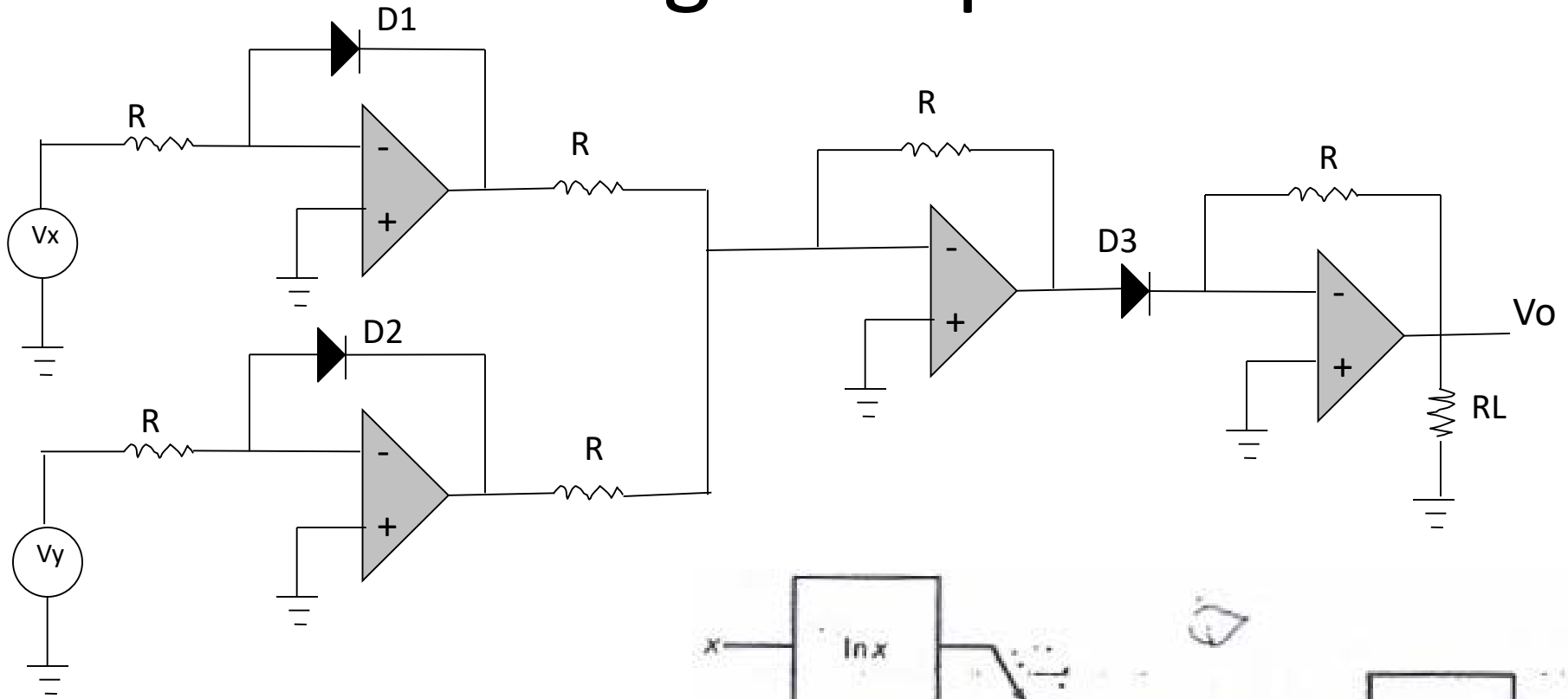


One-quadrant multiplier: inputs must both be of same polarity

Analog Multipliers

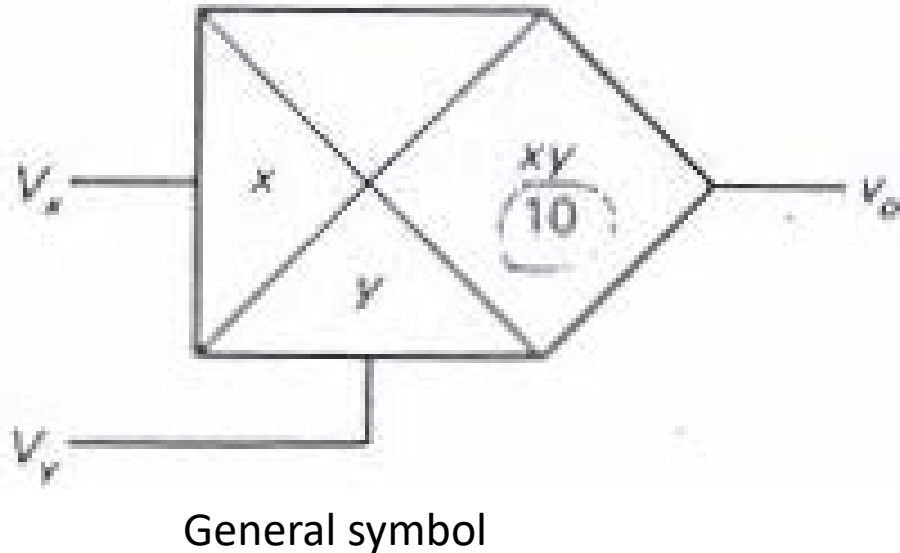

Four quadrants
of operation

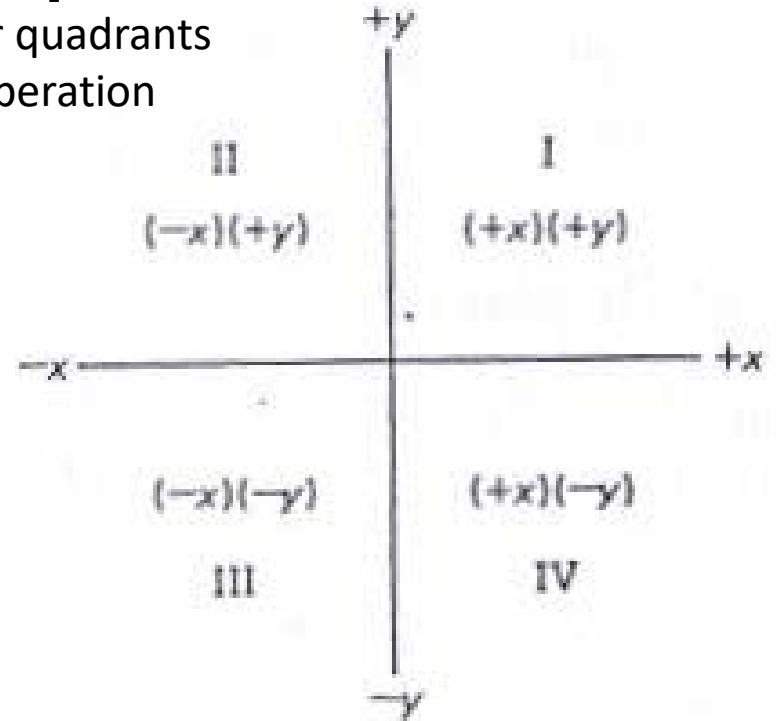


Two-quadrant multiplier: one input should have positive voltages, other input could have positive or negative voltages


Four-quadrant multiplier: any combinations of polarities on their inputs

Analog Multipliers

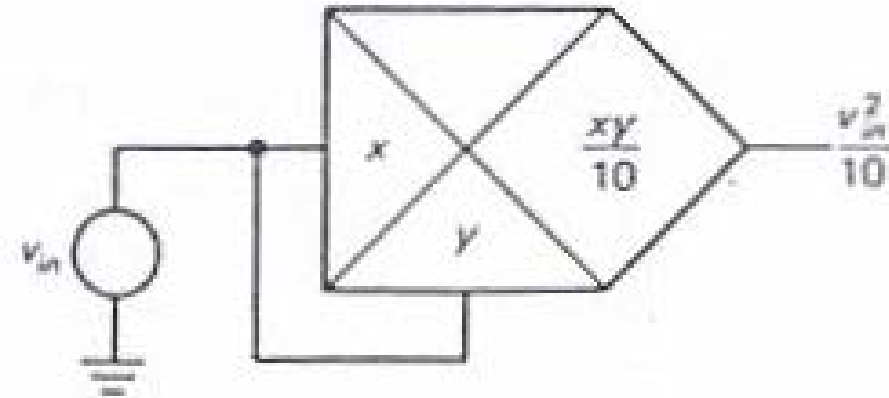Implementation of mathematical operations




Squaring Circuit

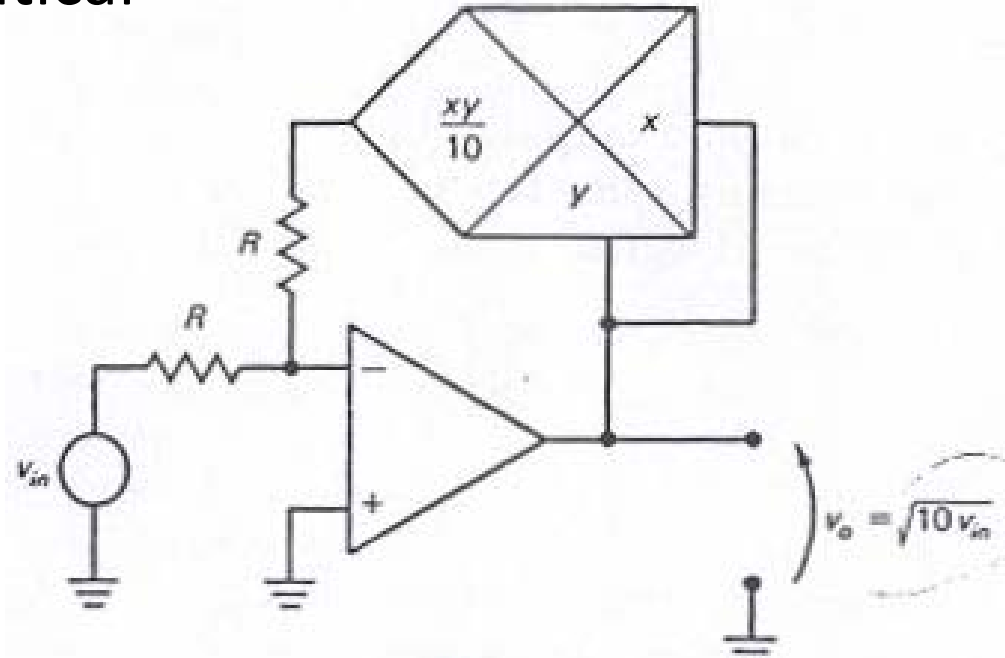


Square root Circuit

Signal Processing

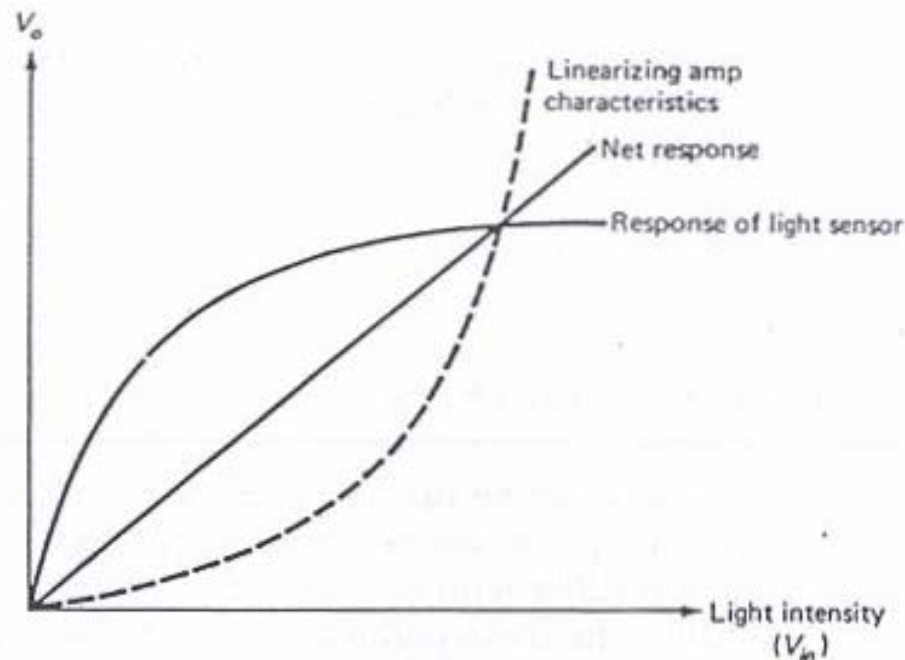- Many transducers produce output voltages that vary nonlinearly with physical quantity being measured (thermistor)
- Often It is desirable to linearize outputs of such devices; logarithmic amps and analog multipliers can be used for such purposes
- Linearization of a signal using circuit with complementary transfer characteristics



Pressure Transmitter

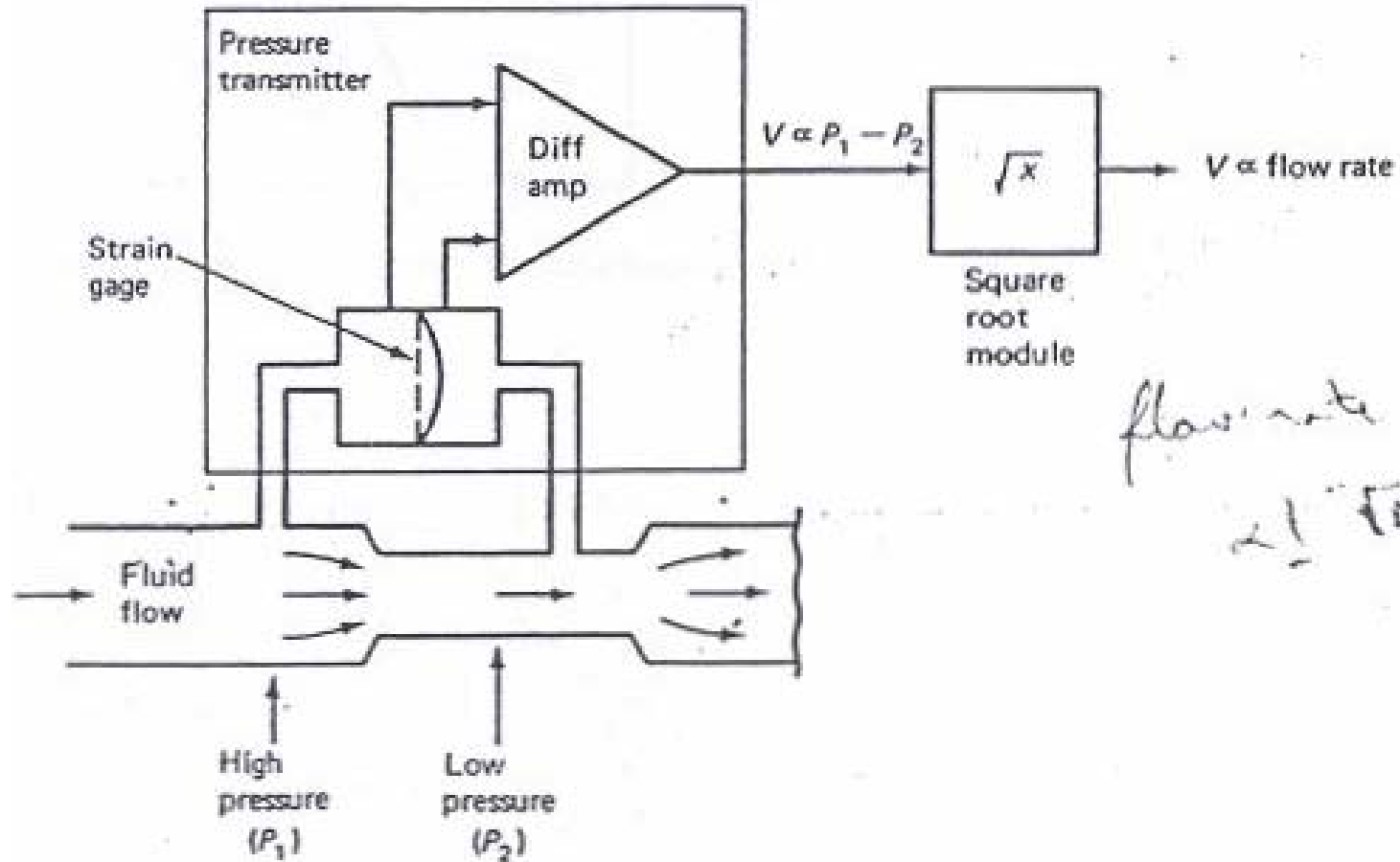


Pressure transmitter produces an output voltage proportional to difference in pressure between two sides of a strain gage sensor

Pressure Transmitter


- A venturi is used to create pressure differential across strain gage
- Output of transmitter is proportional to pressure differential
- Fluid flow through pipe is proportional to square root of pressure differential detected by strain gage
- If output of transmitter is processed through a square root amplifier, an output directly proportional to flow rate is obtained

Precision Rectifiers

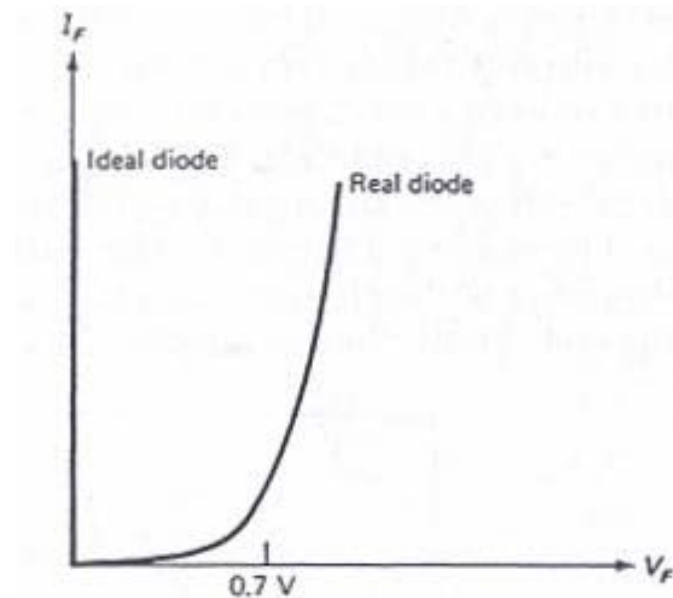- Op amps can be used to form nearly ideal rectifiers (convert ac to dc)
- Idea is to use negative feedback to make op amp behave like a rectifier with near-zero barrier potential and with linear I/O characteristic
- Transconductance curves for typical silicon diode and an ideal diode




Precision Half-Wave Rectifier

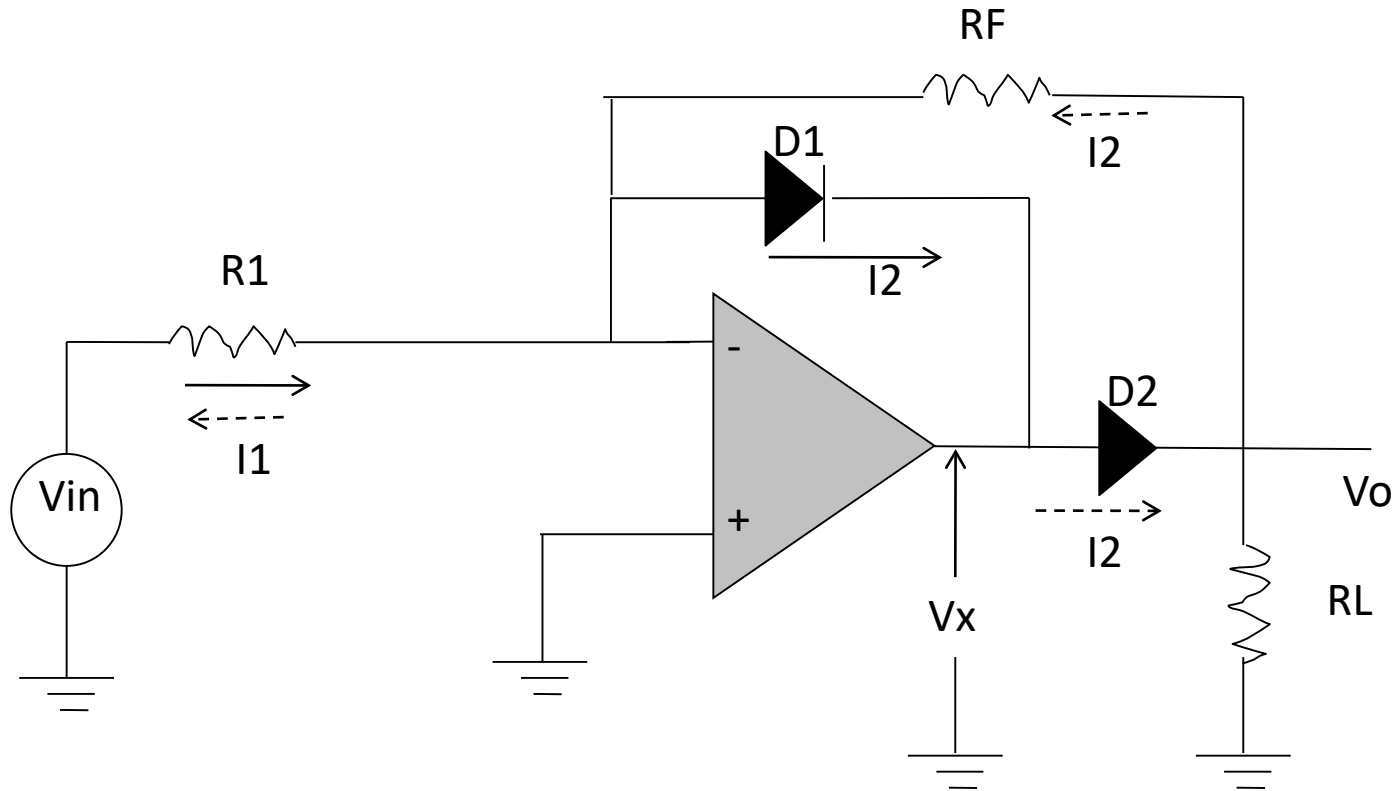


- Solid arrows represent current flow for positive half-cycles of V_{in} and dashed arrows represent current flow for negative half-cycles

Precision Half-Wave Rectifier

- If signal source is going positive, output of op amp begins to go negative, forward biasing D_1
 - Since D_1 is forward biased, output of op amp V_x will reach a maximum level of $\sim -0.7V$ regardless of how far positive V_{in} goes
 - This is insufficient to appreciably forward bias D_2 , and V_o remains at $0V$
- On negative-going half-cycles, D_1 is reverse-biased and D_2 is forward biased
 - Negative feedback reduces barrier potential of D_2 to $0.7V/A_{OL}$ ($\sim = 0$)
 - Gain of circuit to negative-going portions of V_{in} is given by $A_V = -R_F/R_1$

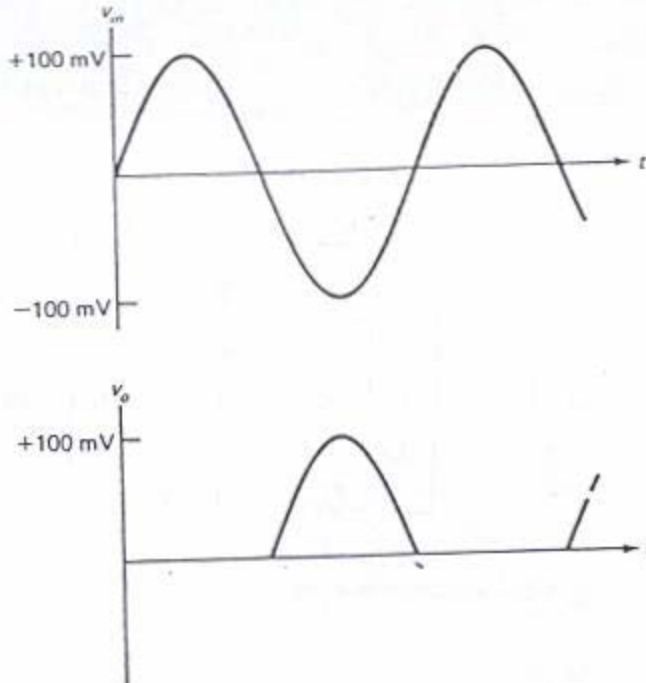

Precision Full-Wave Rectifier

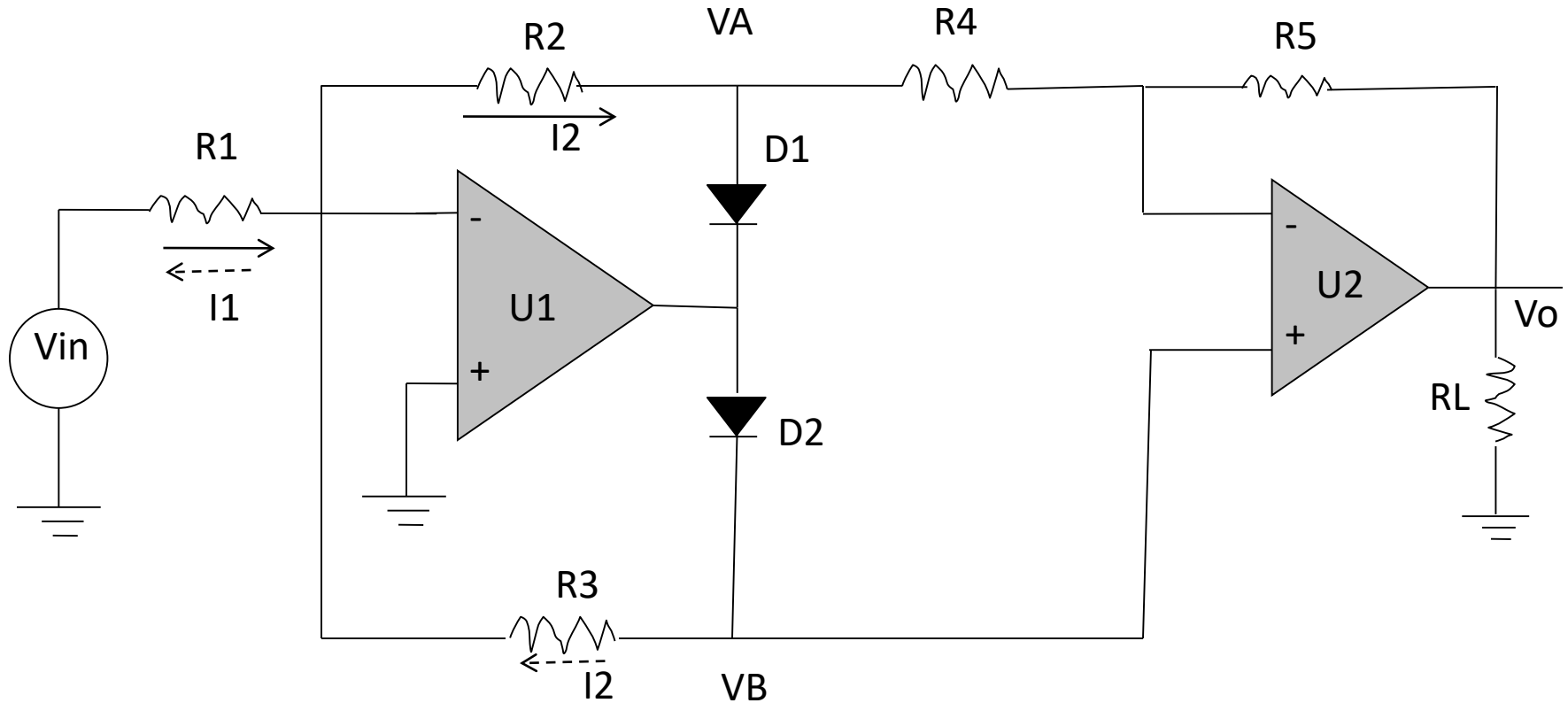

- Solid arrows represent current flow for positive half-cycles of V_{in} and dashed arrows represent current flow for negative half-cycles

Precision Full-Wave Rectifier

- Positive half-cycle causes D_1 to become forward-biased, while reverse-biasing D_2
 - $V_B = 0 \text{ V}$
 - $V_A = -V_{in} R_2/R_1$
 - Output of U_2 is $V_0 = -V_A R_5/R_4 = V_{in} (R_2 R_5/R_1 R_4)$
- Negative half-cycle causes U_1 output positive, forward-biasing D_2 and reverse-biasing D_1
 - $V_A = 0 \text{ V}$
 - $V_B = -V_{in} R_3/R_1$
 - Output of U_2 (noninverting configuration) is
$$V_0 = V_B [1 + (R_5/R_4)] = -V_{in} [(R_3/R_1) + (R_3 R_5/R_1 R_4)]$$
 - if $R_3 = R_1/2$, both half-cycles will receive equal gain

Precision Rectifiers

- Useful when signal to be rectified is very low in amplitude and where good linearity is needed
- Frequency and power handling limitations of op amps limit the use of precision rectifiers to low-power applications (few hundred kHz)
- Precision full-wave rectifier is often referred to as absolute magnitude circuit

ACTIVE FILTERS





Active Filters

- Op amps have wide applications in design of active filters
- Filter is a circuit designed to pass frequencies within a specific range, while rejecting all frequencies that fall outside this range
- Another class of filters are designed to produce an output that is delayed in time or shifted in phase with respect to filter's input
- Passive filters: constructed using only passive components (resistors, capacitors, inductors)
- Active filters: characteristics are augmented using one or more amplifiers; constructed using op amps, resistors, and capacitors only
 - Allow many filter parameters to be adjusted continuously and at will

Filter Fundamentals

- Five basic types of filters
 - Low-pass (LP)
 - High-pass (HP)
 - Bandpass (BP)
 - Bandstop (notch or band-reject)
 - All-pass (or time-delay)

Response Curves

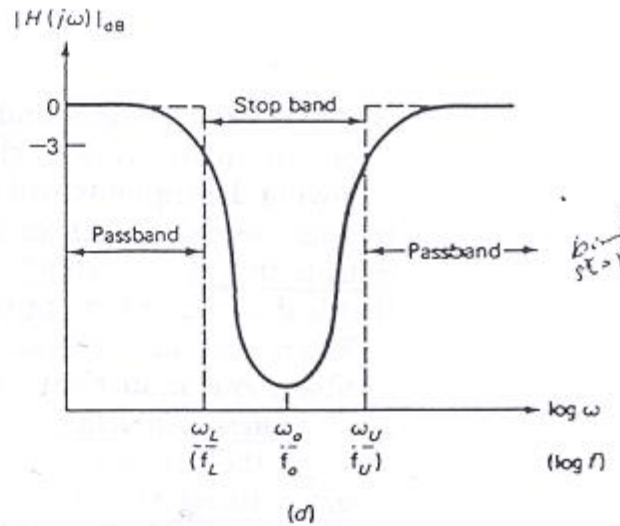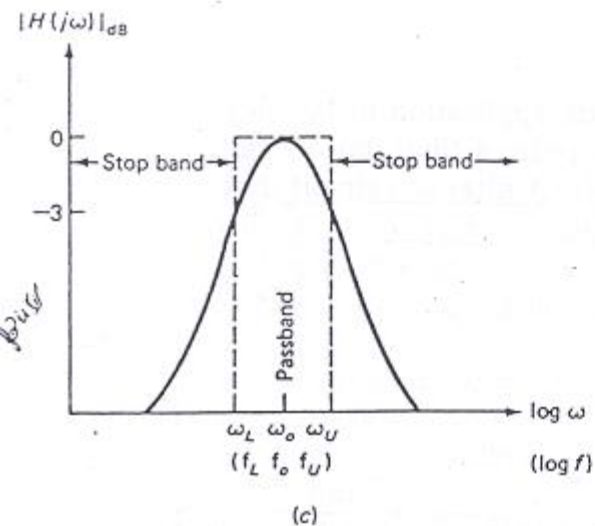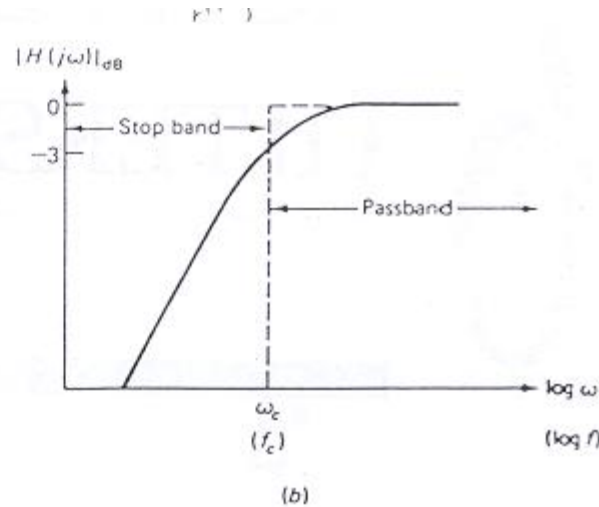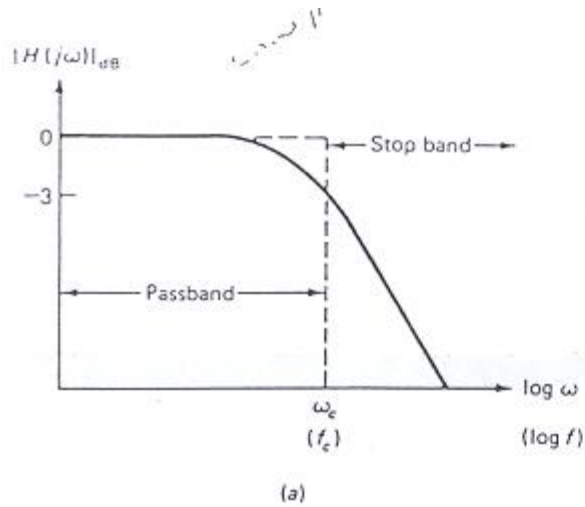

- ω is in rad/s
- $|H(j\omega)|$ denotes frequency-dependent voltage gain of filter
- Complex filter response is given by

$$H(j\omega) = |H(j\omega)| \angle \theta(j\omega)$$

- If signal frequencies are expressed in Hz, filter response is expressed as $|H(jf)|$

Filter Terminology

- Filter passband: range of frequencies a filter will allow to pass, either amplified or relatively unattenuated
- All other frequencies are considered to fall into filter's stop band(s)
- Frequency at which gain of filter drops by 3.01 dB from that of passband determines where stop band begins; this frequency is called corner frequency (f_c)
- Response of filter is down by 3 dB at corner frequency (3 dB decrease in voltage gain translates to a reduction of 50% in power delivered to load driven by filter)
- f_c is often called half-power point

Filter Terminology

- Decibel voltage gain is actually intended to be logarithmic representation of power gain
- Power gain is related to decibel voltage gain as
 - $A_p = 10 \log (P_o/P_{in})$
 - $P_o = (V_o^2/Z_L)$ and $P_{in} = (V_{in}^2/Z_{in})$
 - $A_p = 10 \log [(V_o^2/Z_L) / (V_{in}^2/Z_{in})]$
 - $A_p = 10 \log (V_o^2 Z_{in} / V_{in}^2 Z_L)$
 - If $Z_L = Z_{in}$, $A_p = 10 \log (V_o^2/V_{in}^2) = 10 \log (V_o/V_{in})^2$
 - $A_p = 20 \log (V_o/V_{in}) = 20 \log A_v$
- When input impedance of filter equals impedance of load being driven by filter, power gain is dependent on voltage gain of circuit only


Filter Terminology

- Since we are working with voltage ratios, gain is expressed as voltage gain in dB
 - $|H(j\omega)|_{dB} = 20 \log (V_o/V_{in}) = 20 \log A_V$
- Once frequency is well into stop band, rate of increase of attenuation is constant (dB/decade rolloff)
- Ultimate rolloff rate of a filter is determined by order of that filter
- 1st order filter: rolloff of -20 dB/decade
- 2nd order filter: rolloff of -40 dB/decade
- General formula for rolloff = -20n dB/decade (n is the order of filter)
- Octave is a twofold increase or decrease in frequency
- Rolloff = -6n dB/octave (n is order of filter)

Filter Terminology

- Transition region: region between relatively flat portion of passband and region of constant rolloff in stop band
- Give two filter of same order, if one has a greater initial increase in attenuation in transition region, that filter will have a greater attenuation at any given frequency in stop band
- Damping coefficient (α): parameter that has great effect on shape of LP or HP filter response in passband, stop band, and transition region (0 to 2)
- Filters with lower α tend to exhibit peaking in passband (and stopband) and more rapid and radically varying transition-region response attenuation
- Filters with higher α tend to pass through transition region more smoothly and do not exhibit peaking in passband and stopband


LP Filter Response

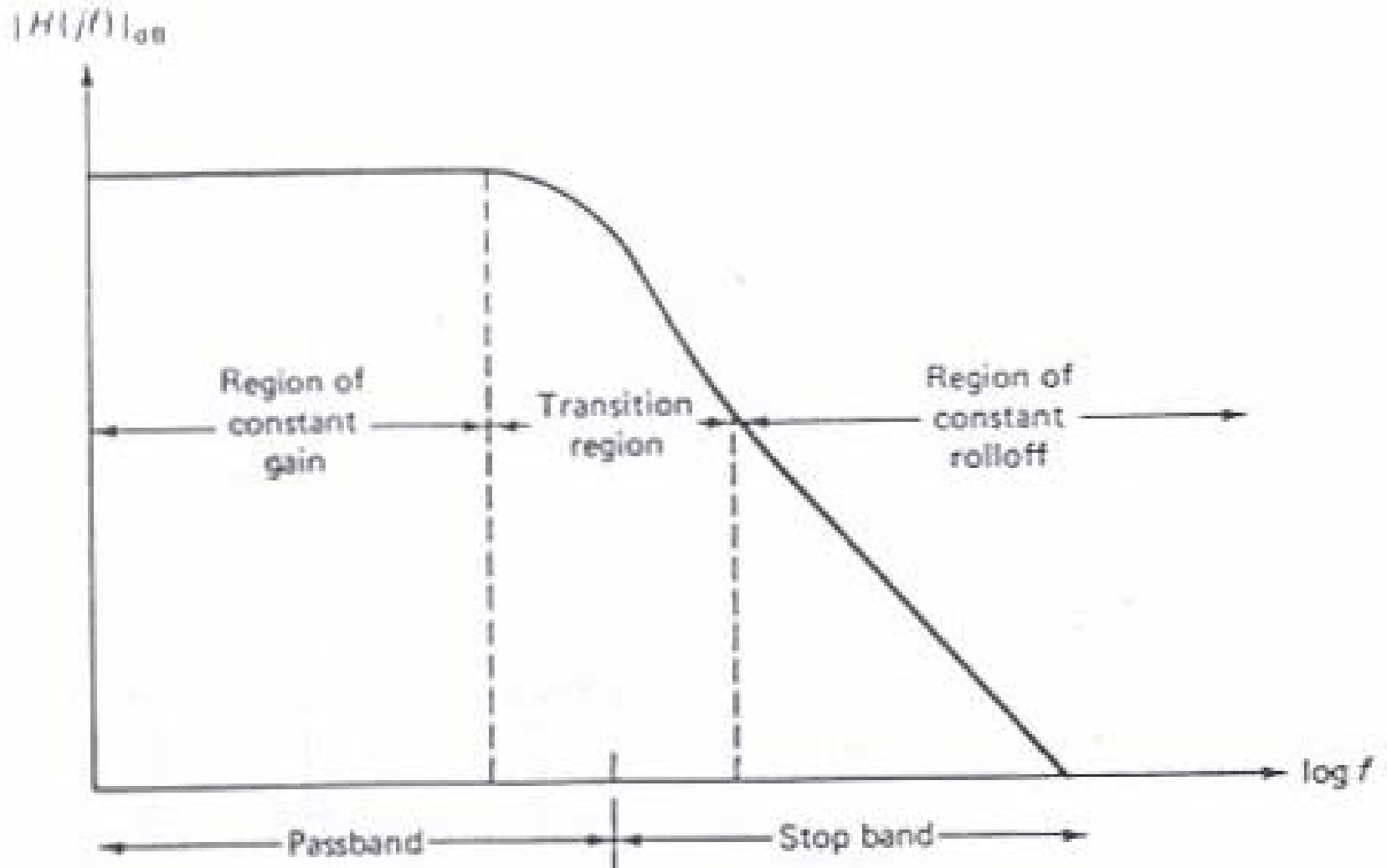


Filter Terminology

- HP and LP filters have single corner frequency
- BP and bandstop filters have two corner frequencies (f_L and f_U) and a third frequency labeled as f_0 (center frequency)
- Center frequency is geometric mean of f_L and f_U
- Due to log f scale, f_0 appears centered between f_L and f_U
$$f_0 = \text{sqrt}(f_L f_U)$$
- Bandwidth of BP or bandstop filter is
$$\text{BW} = f_U - f_L$$
- Also, $Q = f_0 / \text{BW}$ (BP or bandstop filters)
- BP filter with high Q will pass a relatively narrow range of frequencies, while a BP filter with lower Q will pass a wider range of frequencies
- BP filters will exhibit constant ultimate rolloff rate determined by order of the filter

Basic Filter Theory Review

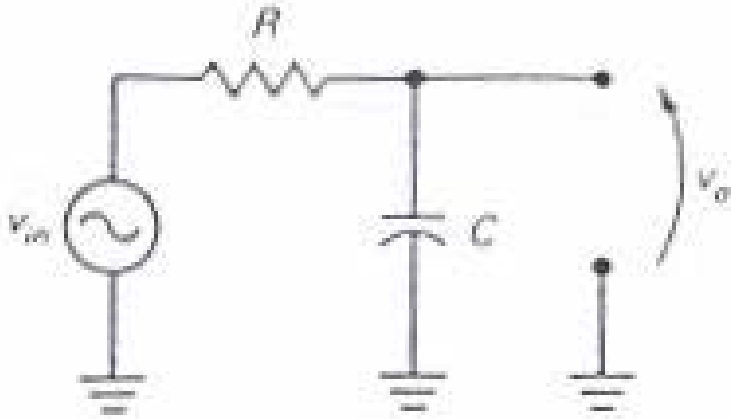

(a)

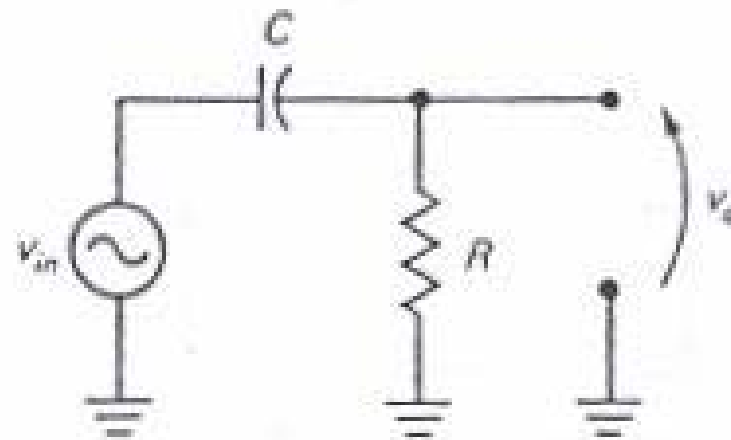

(b)

- Simplest filters are 1st order LP and HP RC sections
 - Passband gain slightly less than unity
- Assuming negligible loading, amplitude response (voltage gain) of LP section is

$$H(j\omega) = (jX_C) / (R + jX_C)$$

$$|H(j\omega)| = X_C / \sqrt{R^2 + X_C^2} < \tan^{-1} (R/X_C)$$
- Corner frequency f_c for 1st order LP or HP RC section is found by making $R = X_C$ and solving for frequency

$$R = X_C = 1/(2\pi fC)$$

$$1/f_c = 2\pi RC$$

$$f_c = 1/(2\pi RC)$$
- Gain (in dB) and phase response of 1st order LP

$$|H(jf)|_{dB} = 20 \log [1/\{\sqrt{1+(f/f_c)^2}\}] < \tan^{-1} (f/f_c)$$
- Gain (in dB) and phase response of 1st order HP

$$|H(jf)|_{dB} = 20 \log [1/\{\sqrt{1+(f_c/f)^2}\}] < \tan^{-1} (f_c/f)$$